



USN

--	--	--	--	--	--	--	--	--	--

14ELE15/25

First/Second Semester B.E. Degree Examination, June/July 2018
Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each module.

Module – 1

- 1 a. State and explain Kirchoff's laws. (06 Marks)
b. A resistor of 2.6Ω is connected in series with a parallel combination of 4Ω and 6Ω resistors. If the power consumed in 4Ω resistor is 36 watts, find :
(i) Voltage across different resistors.
(ii) Source voltage.
(iii) Source current. (08 Marks)
c. Compare and contrast electric and magnetic circuits. (06 Marks)
- 2 a. For the circuit shown in Fig. Q2 (a), find
(i) Current supplied by each battery.
(ii) Total current supplied to 10Ω resistor.
(iii) Total energy delivered to 10Ω resistor, when the circuit is in ON condition for 4 hours. (07 Marks)

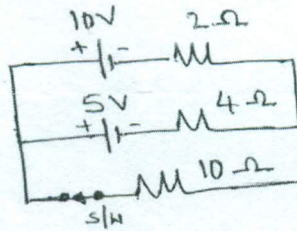


Fig. Q2 (a)

- b. Obtain an expression for energy stored in an inductor. (05 Marks)
c. Two coils X of 12,000 turns and Y of 15,000 turns, lie in parallel planes such that 45% of the flux produced by coil X links coil Y. A current of 5 A in X produces 0.05 wb while the same current in Y produces 0.075 wb. Calculate
(i) The mutual inductance (ii) The coupling coefficient
(iii) The percentage of flux produced by coil Y linking coil X. (08 Marks)

Module – 2

- 3 a. Give a brief classification of dc generators with equivalent circuits. (06 Marks)
b. A 200 V, 4 pole, lap wound dc shunt motor has 800 armature conductors. The resistances of the armature and shunt field windings are 0.5Ω and 200Ω respectively. The motor takes a current of 21A and the flux produced per pole is 30 MWb. Find the speed and gross torque. There is brush contact drop of 1 volt across each brush. (08 Marks)
c. Explain with a neat diagram, the construction and working principle of dynamometer type wattmeter. (06 Marks)
- 4 a. With usual notations, deduce an expression for emf induced in a dc generator. (06 Marks)
b. What is back emf in a dc motor? What is its significance? (04 Marks)
c. Explain, why a series motor should not be started without load over it? (04 Marks)
d. With a neat diagram, explain the construction and working of induction type energy meter. (06 Marks)



14ELE15/25

Module – 3

- 5 a. Explain the following terms:
(i) Peak value (ii) Frequency (06 Marks)
(iii) RMS value with respect to an alternating quantity.
- b. Draw the vector diagram of RLC series circuit when:
(i) Inductive reactance exceeds capacitive reactance. (06 Marks)
(ii) Capacitive reactance exceeds inductive reactance.
(iii) Both inductive and capacitive reactances are equal.
- c. With neat diagram, explain control of a lamp from three different locations. (05 Marks)
- d. What precautions should be taken against electric shock? (03 Marks)
- 6 a. Prove that current in a pure inductive circuit lags behind the applied voltage by 90° . Also draw the power curves. (07 Marks)
- b. A circuit drives a current of $(4+j3)A$ from a $(180+j160)$ volt source. Find the circuit elements, if the supply frequency is 50 Hz. (07 Marks)
- c. Write notes on: (i) Miniature Circuit Breaker (MCB) (06 Marks)
(ii) Earth Leakage Circuit Breaker (ELCB).

Module – 4

- 7 a. What are the advantages of three phase over single phase system? (05 Marks)
- b. Obtain relation between line and phase values of currents in three phase delta system. (07 Marks)
- c. A 12 pole, 500 rpm star connected alternator has 60 slots with 20 conductors/slot. The flux /pole is 0.02 wb which is sinusoidally distributed. The winding factor is 0.97. Calculate frequency and magnitude of line and phase emfs. (08 Marks)
- 8 a. Obtain an expression for power factor angle, when power is measured using two wattmeters. (07 Marks)
- b. Three similar coils each having resistance of 10Ω and inductive reactance of 8Ω are connected in STAR across 400 V, 3 phase supply. Determine (i) Line current (ii) Phase current (iii) Total power and readings of each wattmeter connected to measure power. (07 Marks)
- c. Explain different types of rotors in synchronous generators. (06 Marks)

Module – 5

- 9 a. Show that iron losses and copper losses are equal for maximum efficiency in a transformer. (06 Marks)
- b. A 250 KVA, 1 phase transformer has an efficiency of 98.135% at full load 0.8 lagging power factor. The efficiency was found to be 97.751% at half-full load 0.9 pf. Calculate iron and copper losses. (08 Marks)
- c. Explain the working principle of a 3 phase induction motor. (06 Marks)
- 10 a. Obtain emf equation of transformer. (06 Marks)
- b. Write about various losses that occur in a transformer. (06 Marks)
- c. A four pole, 3 phase induction motor is supplied by 50 Hz AC supply. Find (i) Synchronous speed (ii) Motor speed and (iii) Frequency of rotor induced currents if the slip is 4%. (08 Marks)

* * * * *