

USN

--	--	--	--	--	--	--	--	--	--

17ELE15/25

First/Second Semester B.E. Degree Examination, Feb./Mar. 2022 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. State and explain Kirchhoff's Laws as applied to D.C circuits. (06 Marks)
- b. Define the co-efficient of coupling and find its relation with L_1 , L_2 and M . (06 Marks)
- c. In the circuit shown in Fig Q1(c), what is the voltage across AB if (i) Switch S in open and (ii) Switch S is closed.

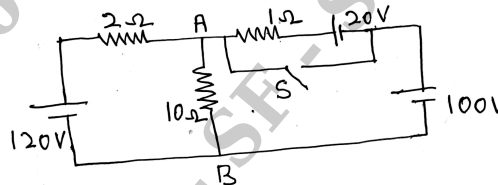


Fig Q1(c)

(08 Marks)

OR

- 2 a. State and explain Faraday's Laws of Electro-magnetic inductions. (06 Marks)
- b. Derive an expression for the energy stored in an inductive coil. (06 Marks)
- c. A circuit consists of two parallel resistors having resistances of 20Ω and 30Ω respectively connected in series with 15Ω . If the current through 15Ω resistor is $3A$, find : i) Current in 20Ω and 30Ω resistor ii) The voltage across the whole circuit iii) The total power and power consumed in all resistances. (08 Marks)

Module-2

- 3 a. Define back emf of D.C motor. What is its significance? (04 Marks)
- b. With a neat sketch, explain the construction of the various parts of a D.C generator. (08 Marks)
- c. With a neat figure, explain the construction and working principle of a dynamometer type Wattmeters. (08 Marks)

OR

- 4 a. Derive the Torque equations of a D.C motor. (06 Marks)
- b. Sketch the various characteristics of D.C shunt and D.C series motor. (06 Marks)
- c. A 4 pole $220V$, lap connected D.C shunt motor has 36 slots, each slot containing 16 conductors; it draws a current of $40A$ from the supply. The field resistance and armature resistances are 110Ω and 0.1Ω respectively. The motor develops an output power of $6kW$. The flux per pole is $40mwb$. Calculate: i) The speed ii) The Torque developed by armature and iii) The shaft torque. (08 Marks)

Module-3

- 5 a. Define and derive an expression for root mean square value of an alternating quantity. (06 Marks)
- b. Derive an equation for the power consumed by an R-L series circuit. Draw the waveform of voltage, current and power and draw the phasor diagram, (08 Marks)
- c. With a neat figure, explain pipe earthing. (06 Marks)



17ELE15/25

OR

- 6 a. With a circuit diagram, explain the working of a two way control of a Lamp. (06 Marks)
- b. A circuit consists of a resistance of a 10Ω , an inductance of 16mH and a capacitance of $150\mu\text{F}$ connected in series. A supply of 100V at 50Hz is given to the circuit. Find the current, p.f and power consumed by the circuit. Draw the vector diagram. (06 Marks)
- c. Two circuits A and B connected in parallel across 200V , 50Hz supply circuit. A consists of 10Ω resistance of 0.12H inductance in series while circuit B consists of 20Ω resistance in series with $40\mu\text{F}$ capacitance. Calculate i) current in each branch ii) Supply current iii) Total power factor. Draw the phasor diagrams. (08 Marks)

Module-4

- 7 a. Derive the emf equation of A.C generator. (06 Marks)
- b. Show that the two Wattmeters are sufficient to measure three phase power. Also derive an expression for the power factor in terms of wattmeter readings. (08 Marks)
- c. When three balanced impedance are connected in star across a 3 phase 415V , 50Hz supply. The line current drawn is 20A , at a Lagging p.f of 0.4 . Determine the parameters of the impedance in each phase. (06 Marks)

OR

- 8 a. In a three phase Delta connection, find the relation between line and phase values of current and voltages. Also derive the equation for three phase power. (06 Marks)
- b. With neat sketches, explain the construction of salient pole alternator. (06 Marks)
- c. A 24 pole turbo alternator has star connected armature winding with 144 slots and 10 conductors per slot, it is driven by a low speed Kaplan turbine at a speed of 250rpm . The winding has full pitched coils with a distribution factor of 0.966 . The flux per pole is 67.3mwb . Determine: i) The frequency and magnitude of line voltage ii) The output KVA of the machine, if the total current in each phase is 50A . (08 Marks)

Module-5

- 9 a. Derive EMF equation of transformer. (06 Marks)
- b. Derive the condition for which the efficiency of a transformer is maximum. (06 Marks)
- c. A 3 phase, 6 pole, 50Hz Induction motor has a slip of 1% at no-load, and 3% at full load. Determine : i) Synchronous speed ii) no-load speed iii) Full load speed iv) Frequency of rotor current at stand still v) Frequency of rotor current at full load. (08 Marks)

OR

- 10 a. Explain clearly the working principle of a three phase induction motor. (06 Marks)
- b. A single phase 20KVA transformer has 1000 primary turns and 2500 secondary turns. The net cross sectional area of the core is 100cm^2 . When the primary winding is connected to 500V 50Hz supply, calculate: i) The maximum flux density in the core ii) The voltage induced in the secondary winding iii) The primary and secondary full load currents. (06 Marks)
- c. A single phase transformer working at 0.8p.f has an efficiency of 94% at both three fourth full load of 600kW . Determine the efficiency at half full load, unity power factor. (08 Marks)
