

# CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

17ELE15/25

## First/Second Semester B.E. Degree Examination, Aug./Sept. 2020 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. State and explain Kirchoff's laws. (06 Marks)
- b. Two coils having 30 and 600 turns respectively are wound side by side on an iron circuit of section  $100\text{cm}^2$  and mean length 150cm
  - i) Estimate the mutual inductance between two coils, if the permeability of iron is 2000
  - ii) A current in the first coil grows steadily from zero to 10A in 0.01sec. Find the emf induced in the other coil. (07 Marks)
- c. An 8 ohms resistor is in series with a parallel combination of two resistors 12 ohms and 6 ohms. If the current in the  $6\Omega$  resistor is 4A. Determine :
  - i) Total current
  - ii) Total supply voltage
  - iii) Total power dissipated in the circuit. (07 Marks)

OR

- 2 a. State and explain : i) Fleming's left hand rule ii) Faraday's second law. (06 Marks)
- b. In the circuit shown in Fig.Q2(b). Find  $E_1$ ,  $E_2$  and  $I$ , when the power dissipated in the  $5\Omega$  resistor is 125W.

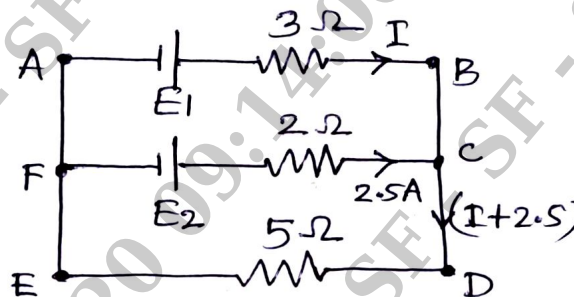


Fig.Q2(b)

- c. Derive an expression for energy stored in a magnetic field. (07 Marks)

### Module-2

- 3 a. Explain the function of following parts of DC machine i) Yoke ii) Field coil iii) Pole core iv) Pole shoe v) Commutator vi) Brush. (06 Marks)
- b. Explain the construction and working principle of dynamometer type wattmeter. (07 Marks)
- c. A 4 pole, 100V DC shunt generator with lap connected armature having field and armature resistance of  $50\Omega$  and  $0.1\Omega$  respectively, supplies sixty 100V, 40W lamps. Calculate :
  - i) Total armature current
  - ii) Current per path
  - iii) Generated EMF. (07 Marks)

OR

- 4 a. Define the Back EMF of a DC motor and explain its significance. (06 Marks)
- b. Explain the basic working principle of a single phase induction type energy meter with a neat diagram. (07 Marks)
- c. A 4 pole DC shunt motor takes 12A from 220V supply. The armature and field resistances are respectively  $0.5\Omega$  and  $100\Omega$ . The armature is lap connected with 300 conductors. If the flux per pole is 20mwb. Calculate : i) Speed ii) Gross torque. (07 Marks)



17ELE15/25

**Module-3**

- 5 a. Derive an expressions for : i) RMS value ii) Average value of sinusoidal AC current. (06 Marks)
- b. Explain the 2 way control of lamp with a suitable circuit diagram and list its applications. (07 Marks)
- c. A  $318\mu\text{F}$  capacitor is connected across a 230 volts, 50Hz AC system. Determine :  
i) Capacitive reactance ii) RMS value of current iii) Equations for voltage and current. (07 Marks)

**OR**

- 6 a. Obtain the voltage and current relations for R–L series AC circuit and show that power  $P = VI \cos \phi$  watts. (06 Marks)
- b. Explain the working of Residual Current Circuit Breaker (RCCB) with a suitable diagram. (07 Marks)
- c. Two impedances  $Z_1 = 2 + j3\Omega$  and  $Z_2 = 2 - j4\Omega$  are connected in parallel, across a 100V, 50Hz AC supply calculate i) branch currents ii) total current of circuit. (07 Marks)

**Module-4**

- 7 a. Explain the generation of 3 phase AC system with suitable diagrams and waveforms. (06 Marks)
- b. A 12 pole, 500RPM, star connected, 3 phase alternator has 48 slots with 15 conductors per slot. The flux per pole is 0.02wb and distributed sinusoidally. The winding factor is 0.97. Calculate : i) Frequency ii) Phase EMF iii) Line EMF. (07 Marks)
- c. Show that two wattmeters are sufficient to measure three phase power and also estimation of power factor. (07 Marks)

**OR**

- 8 a. Explain the constructional features of salient pole type rotor with a neat diagram. (06 Marks)
- b. Three coils each of impedance of  $20\sqrt{60}\Omega$  are connected in star to a 400V, 3phase, 50Hz AC supply. Find the readings on each of two wattmeters connected to measure the input power. (07 Marks)
- c. Derive an EMF equation of a 3 phase alternator. (07 Marks)

**Module-5**

- 9 a. Explain different types of losses in transformer and their minimization techniques. (06 Marks)
- b. Describe the working of STAR – DELTA starter for a 3 phase induction motor with suitable diagram. (07 Marks)
- c. A 30 KVA single phase transformer has a core loss of 450w and full load copper loss of 850w. If the power factor of the load is 0.8. Calculate :  
i) Full load efficiency  
ii) Load for maximum efficiency  
iii) Maximum efficiency at UPF. (07 Marks)

**OR**

- 10 a. Explain the basic working principle of a transformer and list the application of transformer. (06 Marks)
- b. An 8 pole alternator runs at 750RPM and supplies power to a 4 pole induction motor, which runs at 1455RPM. What is the slip of the induction motor? (07 Marks)
- c. Derive an EMF equation of a transformer with suitable notations. (07 Marks)

\* \* \* \* \*