

USN

--	--	--	--	--	--	--	--

18ELE13/23

## First/Second Semester B.E. Degree Examination, Feb./Mar. 2022 Basic Electrical Engineering

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. State and explain Kirchhoff's laws and ohm's law. (06 Marks)  
 b. Find :  
 i) Voltage drop across  $4\ \Omega$   
 ii) Supply voltage for the networks shown in Fig.Q1(b).

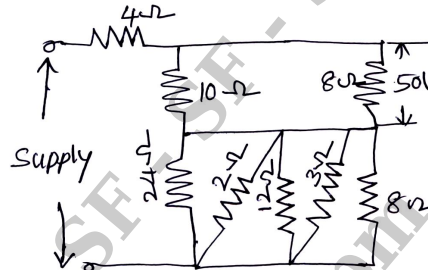


Fig.Q1(b)

- c. Define the following :  
 i) Average value of alternating current    ii) Form factor    iii) Peak factor. (06 Marks)

**OR**

- 2 a. Two resistance  $20\ \Omega$  and  $40\ \Omega$  are connected in parallel. A resistance of  $10\ \Omega$  is connected in series with the combination. A voltage of  $200\text{V}$  is applied across the circuit. Find the current in each resistance and voltage across  $10\ \Omega$ . Find also the power consumed in all the resistors. (08 Marks)  
 b. Derive the expression for RMS value average current of a sinusoidally varying quantity. (08 Marks)  
 c. Two alternating currents in a parallel circuit are represented by  $i_1 = 5\sin \omega t$  and  $i_2 = 10 \sin(\omega t + 60^\circ)$ . Find the resultant current. (04 Marks)

### Module-2

- 3 a. Show that a pure inductance does not consume any power draw the waveforms of voltage, current, power when an alternating voltage is applied to pure inductance. (08 Marks)  
 b. A coil of resistance  $10\ \Omega$  and inductance  $0.1\text{H}$  is connected in series with a  $150\ \mu\text{F}$  capacitor across a  $200\text{V}$ ,  $50\text{Hz}$  supply. Calculate :  
 i) Inductive reactance  
 ii) Capacitive reactance  
 iii) Impedance  
 iv) Current  
 v) Power factor  
 vi) Voltage across coil  
 vii) Voltage across capacitor. (08 Marks)  
 c. An inductive coil takes a current of  $33.24\text{a}$  from  $230\text{V}$ ,  $50\text{Hz}$  supply, if the resistance of coil is  $6\ \Omega$ . Calculate inductance of the coil and power taken by the coil. (04 Marks)



18ELE13/23

OR

- 4 a. In a three phase star connection, show that  $V_L = \sqrt{3}V_{ph}$ , also draw vector diagram of line voltage and phase voltage. (07 Marks)
- b. What are the advantages and three phase system over a single phase system? (07 Marks)
- c. A delta connected load consist of a resistance of  $10\Omega$  and capacitance of  $100\mu F$  in each phase. A supply of 410V at 50Hz a applied to the load. Find line current, power consumed by the load and power factor. (06 Marks)

**Module-3**

- 5 a. Derive the EMF equation of a transformer. (06 Marks)
- b. A single phase transformer working at 0.8 power factor has an efficiency at 94% at both  $\frac{3}{4}$  full load and pull load of 600KW. Find the efficiency at  $\frac{1}{2}$  full load unity power factor. (08 Marks)
- c. Primary winding of a transformer is connected to a 240V, 50Hz. The secondary winding has 1500 turns and the maximum value of core flux is 0.00207  $\omega b$ . Find secondary induced emf, number of turns in primary and cross sectional area of core. If max value of flux density is 0.465 Tesla. (06 Marks)

OR

- 6 a. Explain plate Earthing. (06 Marks)
- b. With circuit diagram and switching table, explain two-way control of lamp. (08 Marks)
- c. What are the precaution to be taken against electric shock? (06 Marks)

**Module-4**

- 7 a. Draw a neat sketch of DC machine and name the parts and briefly explain the function of each. (10 Marks)
- b. A 4-pole, 220V, Lap connected DC shunt motor has 36 slots, each slot containing 16 conductors, it draws a current of 40A from the supply. The field resistance and armature resistance are  $110\Omega$  and  $0.1\Omega$  respectively. The motor develops an output power of 6KW. Flux per pole is 40MWb. Calculate : i) speed ii) torque developed by the armature iii) shaft torque. (10 Marks)

OR

- 8 a. EMF generated in the armature of a shunt generator is 625V. When delivering its full current of 400A to an external circuit. The field current is 6A and armature resistance is  $0.06\Omega$ . What is the terminal voltage? (06 Marks)
- b. Sketch the various characteristic of DC motor (shunt). (08 Marks)
- c. What is the significance of back EMF in a DC motor? (06 Marks)

**Module-5**

- 9 a. Derive the EMF equation of an alternator. (06 Marks)
- b. 4-pole, 1500rpm, star connected alternator has 9 slot/pole, and 8 conductor per slot. Find the flux per pole to give a terminal voltage of 3300V. Take the winding factor as unity. (07 Marks)
- c. A 6 pole, star connected alternator has a 90 slot and 8 conductor per slot, and rotates at 1000rpm. The flux per pole is 50 mwb. Find the induced emf across its lines. Take the winding factor of 0.97. (07 Marks)

OR

- 10 a. Mention the advantages and disadvantages of a squirrel cage and slip ring induction motors. (07 Marks)
- b. Why starter is required for a three phase induction motor? (07 Marks)
- c. A 6 pole induction motor is supplied by a 10 pole alternator. Which is driven at 600rpm. If the motor is running at 970rpm, find the slip. (06 Marks)