

USN

--	--	--	--	--	--	--	--	--	--



10ES32

Third Semester B.E. Degree Examination, June/July 2015
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. State and explain the various resistance levels of the semiconductor diode. (06 Marks)
- b. Explain the working of a full wave centre tapped rectifier. Also determine ripple factor, efficiency and voltage regulation. (10 Marks)
- c. Design a suitable circuit represented by the box shown below, which has the input and output waveforms as indicated. (04 Marks)

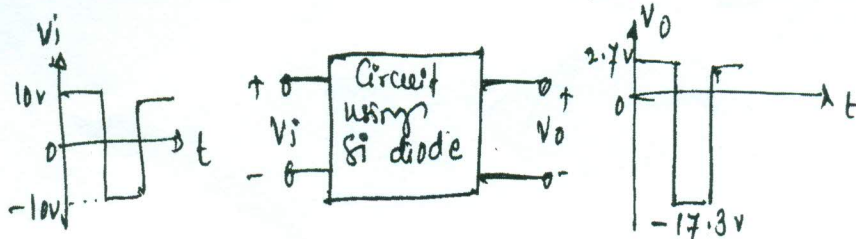


Fig. Q1(c)

- 2 a. Name different biasing methods of transistor. With circuit diagram analyze the fixed bias circuit, with effect of variation in I_B , R_C and V_{CC} on Q. point of the load line. (10 Marks)
- b. Explain the circuit of a transistor switch being used as an inverter. (04 Marks)
- c. In a voltage divider bias circuit of BJT. $V_{CC} = 20\text{ V}$, $R_C = 10\text{ k}\Omega$, $R_E = 1.5\text{ k}\Omega$, $R_1 = 40\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$. Assume silicon transistor with $\beta = 150$. Find I_C , V_{CE} and $I_{C(sat)}$ using exact analysis. (06 Marks)
- 3 a. Define h – parameters and hence derive h – parameters model of CE – BIT. (06 Marks)
- b. Explain with a neat circuit diagram of emitter follower configuration. Justify how voltage gain is nearly equal to one. (06 Marks)
- c. For the circuit shown below determine V_{CC} , if $A_V = -160$ and $r_0 = 100\text{ k}\Omega$. Take $\beta = 100$. (08 Marks)

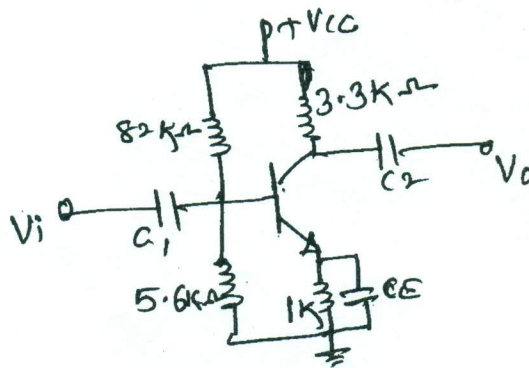


Fig. Q3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.



- 4 a. Draw the single stage RC coupled BJT amplifier and discuss the effect of (low frequency response) : i) Input capacitance C_S ii) output capacitance C_C and iii) Emitter bypass capacitance C_e on frequency response. (05 Marks)
- b. Prove that miller effect of input capacitance $C_{Mi} = (1 - A_v) C_f$ and output capacitance $C_{Mo} = \left(1 - \frac{1}{A_v}\right) C_f$. (10 Marks)
- c. It is desired that the voltage gain of an RC - coupled amplifier at 60 Hz should not decrease by more than 10% from its mid band value. Calculate :
i) the lower 3 dB frequency
ii) the required C if $R = 2000 \Omega$. (05 Marks)

PART - B

- 5 a. Derive expressions for Z_i and A_i for a Darlington emitter follower circuit. (10 Marks)
- b. Mention the types of feedback connections. Draw their block diagrams indicating input and output signal. (06 Marks)
- c. List the general characteristics of a negative feedback amplifier and write its advantages. (04 Marks)
- 6 a. With a neat circuit diagram, explain the operation of a transformer coupled class A power amplifier. (07 Marks)
- b. Explain the operation of a class B push-pull amplifier and derive its conversion efficiency. (08 Marks)
- c. The following distortion reading are available for a power amplifier :
 $D_2 = 0.2$, $D_3 = 0.02$, $D_4 = 0.06$, with $I_1 = 3.3A$ and $R_C = 4 \Omega$. Calculate :
i) the THD ii) the fundamental power component iii) the total power. (05 Marks)
- 7 a. Explain the working of Wien bridge oscillator. (07 Marks)
- b. With a neat circuit diagram, explain the operation of BJT Colpitts oscillator. (06 Marks)
- c. A crystal has the following parameter $L = 0.334 H$, $C_M = 1 pF$, $C = 0.065$ and $R = 5.5 k\Omega$. Calculate the series resonant frequency, parallel resonant frequency and find Q of the crystal. (07 Marks)
- 8 a. Draw the JFET common drain configuration (source - follower) circuit. Derive Z_i , Z_o and A_v using small signal model. Write its characteristics. (10 Marks)
- b. Compare JFET and MOSFET. (03 Marks)
- c. For the JFET common drain configuration shown below. Given $I_{dss} = 10 mA$, $V_P = -5V$, $r_d = 40 k\Omega$, $V_{GSQ} = -2.85 V$ i) Calculate Z_i and Z_o ii) Calculate A_v iii) find V_o if $V_i = 20 mV$ (p - p). (07 Marks)

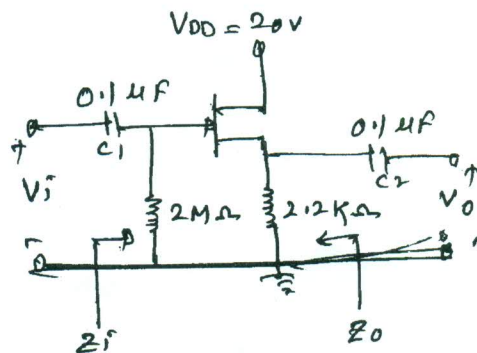


Fig. Q8(c)
