

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



10ES33

Third Semester B.E. Degree Examination, Dec.2015/Jan.2016
Logic Design

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART - A

- 1 a. Define combinational logic. Two motors M_2 and M_1 are controlled by three sensors S_1 , S_2 and S_3 . One motor M_2 is to run any time when all three sensors are on. The other motor (M_1) is to run whenever sensors S_2 or S_1 but not both are on and S_3 is off. For all sensors combinations where M_1 is on, M_2 is to be off, except when all sensors are off and then both motors remain off. Construct the truth table and write the Boolean output equation. (05 Marks)
- b. The following Boolean function into their proper canonical form in decimal notation.
 - i) $M = p(q' + s)$
 - ii) $N = (w' + x)(y + z)$ (07 Marks)
- c. Reduce the following Boolean function using K-map and realize the simplified expression using NAND gates. (08 Marks)

$$T = f(a, b, c, d) = \sum m(1, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$$
- 2 a. Simplify the following function using Quine-McClusky method and realize the simplified using NOR gates. (12 Marks)

$$P = f(w, x, y, z) = \sum m(7, 9, 12, 13, 14, 15) + \sum d(4, 11)$$
- b. Simplify $f(a, b, c, d) = \sum m(0, 4, 5, 6, 13, 14, 15) + \sum d(2, 7, 8, 9)$ using MEV technique using basic gates. (08 Marks)
- 3 a. Design a combinational circuit to find the 9's complement of a single digit BCD number. Realize the circuit using suitable logic gates. (08 Marks)
- b. Draw the logic diagram for 2 to 4 line decoder with an active low encoder enable and active high data output. Construct a truth table and describe the circuit function with logic symbol (74139IC's) for the decoder. (06 Marks)
- c. Design a 4 to 16 line decoder using 2 to 4 line decoder which has the active low outputs and active low enable input. Explain its operation. (06 Marks)
- 4 a. Design a binary full adder using only two input NAND gates. Write a truth table. (06 Marks)
- b. Implement the following Boolean function using 4 : 1 multiplexer (MUX)

$$Y = f(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$$
 (06 Marks)
- c. Define magnitude comparator. Design a two-bit binary comparator and implement with suitable logic gates. (08 Marks)

PART - B

- 5 a. Discuss the difference between a flip flop and latch. Explain the operation of gated SR latch with a logic diagram, truth table and logic symbol. (06 Marks)
- b. Explain the working of Master Slave JK flip flops with functional table and timing diagram. Show how race around condition is overcome. (08 Marks)
- c. Obtain the characteristic equation of JK and SR flipflops. (06 Marks)

Important Note : 1. On completing your answers, carefully draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8=50, to be treated as malpractice.



- 6 a. Describe the block diagram of a MOD-6 twisted ring counter and explain its operation with the count sequence table and decoding logic used to identify the various states. (08 Marks)
- b. Design a mod-6 synchronous counter using clocked JK flipflops, the count sequence being 0, 2, 3, 6, 5, 1, 0, 2..... (12 Marks)

- 7 a. With a suitable block diagram, explain the Mealy and Moore model, in a sequential circuit analysis. (10 Marks)
- b. Explain 4 bit universal shift Register using 4 : 1 MUX with help of logic diagram. Write a mode control table. (10 Marks)

- 8 a. Describe the following terms with respect to sequential machines:
i) State ii) Present states iii) Next states. (06 Marks)
- b. A sequential circuit has one input one output. The state diagram is shown in Fig. Q8 (b). Design a sequential circuit with T flip flops. (14 Marks)

 


Fig. Q8 (b)

Highly confidential document