

# CBCS SCHEME



15EC33

USN

--	--	--	--	--	--	--	--	--	--

## Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Define combinational logic. Design a combinational circuit which takes two, 2 bit binary numbers as its input and generates an output equal to 1, when the sum of the two numbers is even. (10 Marks)
- b. Simplify using Karnaugh map. Write the Boolean equation and realize using NAND gates.  
 $D = f(w, x, y, z) = \sum m(0, 2, 4, 6, 8) + \sum d(10, 11, 12, 13, 14, 15)$ . (06 Marks)

OR

- 2 a. Define canonical SOP and canonical POS. Expand  $f = (\bar{a} + b + c)(a + c + \bar{d})$  into canonical POS. (04 Marks)
- b. Solve using Quine-McCluskey tabulation method,  
 $f(a, b, c, d) = \sum m(0, 1, 4, 5, 9, 10, 12, 14, 15) + \sum \phi(2, 8, 13)$   
Obtain the minimal form of the given function. Verify the result using k-map. (12 Marks)

### Module-2

- 3 a. Define decoder. Implement full subtractor using a decodes. Write the truth table. (08 Marks)
- b. Compare ripple carry adder and look ahead carry adder. Explain the circuit and operation of a 4 bit binary adder with look ahead carry. (08 Marks)

OR

- 4 a. Design and implement one bit comparator. (04 Marks)
- b. Implement the multiple functions :  
 $f_1(a, b, c, d) = \sum(0, 4, 8, 10, 14, 15)$  and  
 $f_2(a, b, c, d) = \sum(3, 7, 9, 13)$   
using two 3 to 8 decoders, i.e. 74138 ICs. (06 Marks)
- c. Implement full adder circuit using 8 : 1 multiplexer. (06 Marks)

### Module-3

- 5 a. What is gated SR Latch? Explain the operation of gated SR Latch, with a logic diagram, truth table and logic symbol. (08 Marks)
- b. Derive the characteristic equation of SR, JK, D and T flip-flops with the help of function tables. (08 Marks)

OR

- 6 a. Explain the operation of a switch debouncer built using SR Latch. Draw the supporting waveforms. (04 Marks)
- b. Explain 0s and 1s catching problem of Master Slave JK flip flop with waveform. Suggest the solution for this problem. (04 Marks)
- c. What is edge triggered flip flop? With a neat circuit diagram, explain the operation of positive edge triggered D flip flop, using NAND gates. (08 Marks)

**Module-4**

- 7 a. With the help of neat diagram, explain PISO and PIPO operation of unidirectional shift registers. (08 Marks)
- b. Design a 4 bit binary ripple 'UP' counter using negative edge triggered JK flip flop. Show the up counter execution with the help of timing diagram. (08 Marks)

OR

- 8 a. Implement a Mod 8 twisted ring counter using D flip flops. Give the counting sequence and decoding gate inputs. (06 Marks)
- b. Design a synchronous MOD-6 counter using JK flip flop for the following count sequence 0, 2, 3, 6, 5, 1 and repeat. Write the transition table, logic equations and the counter implementation diagram. (10 Marks)

**Module-5**

- 9 a. Compare Mealy and Moore sequential circuit models with suitable example. (04 Marks)
- b. For the logic diagram shown in Fig.Q9(b), write the state and output equations. Give the transition table and the state diagram. (12 Marks)

 


Fig.Q9(b)

OR

- 10 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
- b. How to convert a Mealy machine to a Moore machine? (02 Marks)
- c. A sequential circuit has one input and one output. The state diagram is shown in Fig.Q10(c). Design a sequential circuit using D flip flop. (08 Marks)

 


Fig.Q10(c)

\*\*\*\*\*