



15EC35

OR

- 4 a. Explain digital frequency meter with the help of block diagram. (08 Marks)
b. Explain digital pH meter. (08 Marks)

Module-3

- 5 a. Explain the function of various blocks in CRO with suitable diagram. (06 Marks)
b. Explain the working of Time base generator. (06 Marks)
c. Discuss frequency measurements with Lissajous figures. (04 Marks)

OR

- 6 a. Explain function generator with suitable diagram. (08 Marks)
b. Explain sweep generator with block diagram. (08 Marks)

Module-4

- 7 a. Explain Q-meter with suitable circuit diagram. (06 Marks)
b. Explain Basic Megger Circuit. (06 Marks)
c. Discuss stroboscope. (04 Marks)

OR

- 8 a. Explain the Wheatstone bridge and using Thevenin's theorem, determines the amount of deflection due to unbalance of Wheatstone Bridge. (08 Marks)
b. An inductance comparison bridge is used to measure inductive impedance at a frequency of 5KHz. The bridge constants at balance are $L_3 = 10\text{mH}$, $R_1 = 10\text{k}\Omega$, $R_2 = 40\text{k}\Omega$, $R_3 = 100\text{k}\Omega$. Find the equivalent series circuit of the unknown impedance. (04 Marks)
c. Write a note on Wagner's earth connection. (04 Marks)

Module-5

- 9 a. What are the factors to be considered for the selection of better transducer? (04 Marks)
b. Derive an expression for gauge factor for Bonded Resistance wire strain Gauges. (08 Marks)
c. Mention advantages and limitation of thermistor. (04 Marks)

OR

- 10 a. Explain the construction, principle and operation of LVDT. Show characteristics curve. (10 Marks)
b. Explain Piezoelectric Transducer. (06 Marks)

* * * * *