



USN

--	--	--	--	--	--	--	--

17EC35

Third Semester B.E. Degree Examination, July/August 2021 Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1 a. Using source transformation techniques, find 'v' for the circuit in Fig.Q1(a).

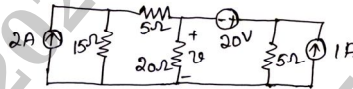


Fig.Q1(a)

(07 Marks)

- b. Obtain equivalent resistance R_{ab} for the circuit in Fig.Q1(b) and hence find 'i'.

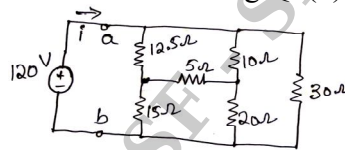


Fig.Q1(b)

(07 Marks)

- c. Explain ideal and practical current sources.

(06 Marks)

- 2 a. Determine the current I_0 in the circuit of Fig.Q2(a) using Mesh analysis.

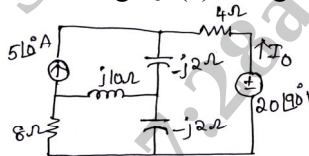


Fig.Q2(a)

(08 Marks)

- b. Use nodal analysis to find v_0 in the network of Fig.Q2(b).

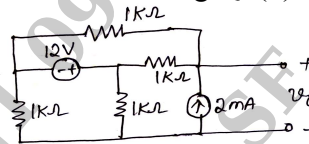


Fig.Q2(b)

(08 Marks)

- c. Explain the concept of super node with an illustration.

(04 Marks)

- 3 a. State and prove Reciprocity theorem.

(06 Marks)

- b. Use superposition theorem to find i_0 in the circuit shown in Fig.Q3(b).

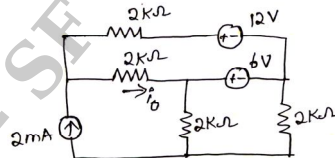


Fig.Q3(b)

(06 Marks)

- c. Find Thevenin's equivalent circuit across the terminals a – b for the circuit shown in Fig.Q3(c).

(08 Marks)

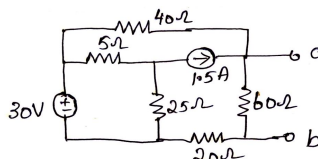


Fig.Q3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8=50, will be treated as malpractice.

- 4 a. State and prove maximum power transfer theorem for the case of AC source, hence show that
$$P_{\max} = \frac{|V_{\text{TH}}|^2}{8R_L}$$
 (08 Marks)

- b. Find the current through 16Ω resistor using Norton's theorem in Fig.Q4(b).

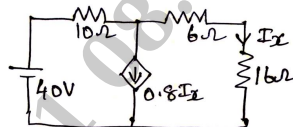


Fig.Q4(b)

(08 Marks)

- c. Find the current through $(10 - 3j)\Omega$ using Millman's theorem in Fig.Q4(c).

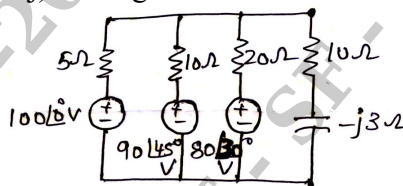


Fig.Q4(c)

(04 Marks)

- 5 a. The switch 'K' is changed from position 1 to position 2 at $t = 0$. Steady state condition having been reached at position 1. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. [Refer Fig.Q5(a)] (06 Marks)

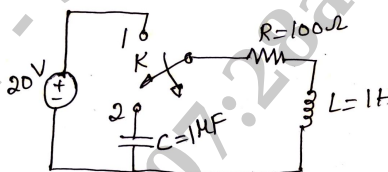


Fig.Q5(a)

- b. In the network shown in Fig.Q5(b), $V_1(t) = e^{-t}$ for $t \geq 0$ and is zero for all $t < 0$. If the capacitor is initially uncharged. Determine the value of $\frac{d^2V_2}{dt^2}$ and $\frac{d^3V_2}{dt^3}$ at $t = 0^+$.

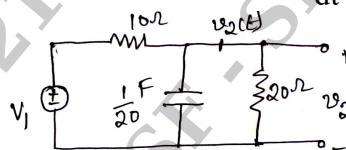


Fig.Q5(b)

(08 Marks)

- c. Explain initial and final conditions in case of a capacitor. (06 Marks)

- 6 a. For the circuit shown in Fig.Q6(a),
 (i) Find the differential equation for $i_L(t)$
 (ii) Find Laplace transform of $i_L(t)$
 (iii) Solve for $i_L(t)$

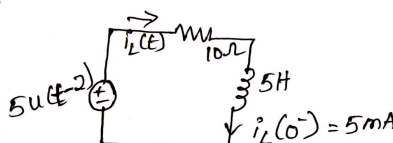


Fig.Q6(a)

(08 Marks)

- b. For the circuit shown in Fig.Q6(b), (i) Find the differential equation for $i_L(t)$, (ii) Find Laplace transform of $i_c(t)$, (iii) Solve for $i_L(t)$. (08 Marks)

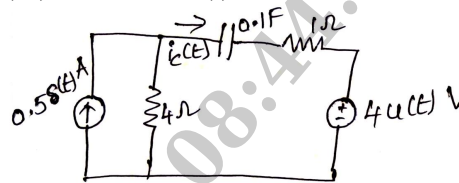


Fig.Q6(b)

- c. Obtain Laplace transform for a decaying exponential signal. (04 Marks)
- 7 a. Prove that the resonant frequency is the geometric mean of the two half power frequencies i.e., Show that $\omega_0 = \sqrt{\omega_1\omega_2}$ (08 Marks)
- b. Obtain an expression for quality factor of an capacitor. (07 Marks)
- c. In a series circuit, $R = 6 \Omega$, $\omega_0 = 4.1 \times 10^6$ rad/sec, bandwidth = 10^5 rad/sec. Compute L, C half power frequencies and Q. (05 Marks)
- 8 a. Obtain an expression for the resonant frequency in a parallel resonant circuit. (08 Marks)
- b. Show that a two branch parallel resonant circuit is resonant at all frequencies when
- $$R_L = R_C = \sqrt{\frac{L}{C}} \quad (07 \text{ Marks})$$
- c. Find the value of R_L for which the circuit is at resonance, as shown in Fig.Q8(c). (05 Marks)

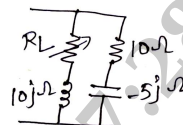


Fig.Q8(c)

- 9 a. Obtain an expression for h-parameters in terms of Z-parameters. (08 Marks)
- b. Find Z and Y parameters for the network shown in Fig.Q9(b). (08 Marks)

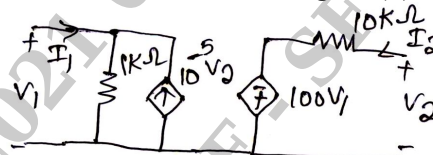


Fig.Q9(b)

- c. Explain ABCD parameters. (04 Marks)
- 10 a. Obtain an expression for Y-parameters in terms of ABCD parameters. (08 Marks)
- b. Find ABCD parameters for the network shown in Fig.Q10(b).

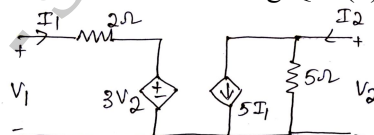


Fig.Q10(b)

- c. State reciprocity condition for
- (i) Z – parameters
 - (ii) Y – parameters
 - (iii) h – parameters
 - (iv) ABCD – parameters
- (04 Marks)
