



USN

--	--	--	--	--	--	--	--	--	--

18EC34

Third Semester B.E. Degree Examination, July/August 2021 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1
 - a. Define combinational logic circuit and place the following equation into the proper canonical form:
 $P = f(a, b, c) = ab' + ac' + bc$ (04 Marks)
 - b. Obtain minimal expression using k-map for the following incompletely specified function:
 $F(a, b, c, d) = \sum m(0, 1, 4, 6, 7, 9, 15) + \sum d(3, 5, 11, 13)$ and draw the circuit diagram using basic gates. (06 Marks)
 - c. Minimize the expression using Quine Mecluskey method.
 $Y = \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}C\overline{D} + A\overline{B}CD + A\overline{B}C\overline{D} + \overline{A}B\overline{C}D$ (10 Marks)

- 2
 - a. Place the following equations into the proper canonical form:
 - i) $G = f(w, x, y, z) = \overline{w}x + y\overline{z}$
 - ii) $T = f(a, b, c) = (a + \overline{b})(\overline{b} + c)$ (04 Marks)
 - b. Obtain minimal logical expression for the given maxterm expression using K-map
 $f(a, b, c, d) = \pi M(0, 1, 4, 5, 6, 7, 9, 14) \cdot \pi d(13, 15)$. (06 Marks)
 - c. Obtain all the prime implicants of the following Boolean function using Quine-Meckluskey method
 $f(a, b, c, d) = \sum(0, 2, 3, 5, 8, 10, 11)$. Verify the result using K map technique. (10 Marks)

- 3
 - a. Draw the circuit for 3 to 8 decoder and explain. (08 Marks)
 - b. Implement the following Boolean function using 4:1 multiplexer.
 $F[A, B, C, D] = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$. (06 Marks)
 - c. A combinational circuit is defined by the functions $F_1 = \sum m(3, 5, 7)$, $F_2 = \sum m(4, 5, 7)$. Implement the circuit with a programmable logic array having 3 inputs, 3 product terms and two outputs. (06 Marks)

- 4
 - a. Draw the key pad interfacing diagram to a digital system using 10-line decimal to BCD encoder and explain. (06 Marks)
 - b. Explain Look-Ahead carry adder with neat diagram and relevant expression. (06 Marks)
 - c. Design 2-bit comparator using gates. (08 Marks)

- 5
 - a. Explain the operation of a switch debouncer using S-R. Latch with the help of circuit and waveforms. (06 Marks)
 - b. Find characteristic equations for S-R and T. Flip flops with the help of function tables and explain. (06 Marks)
 - c. Explain the working principle of 4-bit synchronous binary counts. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 6 a. Draw the logic diagram, functional table and timing diagram of master-slave JK flip flop and explain briefly. (10 Marks)
- b. Explain four bit binary ripple counter with logic and timing diagram. (10 Marks)

- 7 a. Design mod-6 synchronous counter by using JK flip-flop, with excitation table. (10 Marks)
- b. Draw and explain Mealy and Moore sequential circuit model and compare mealy and Moore circuit models. (10 Marks)

- 8 a. Design a Mod-6 synchronous counter using clocked T Flip-Flop. (10 Marks)
- b. Construct the transition table, state table and state diagram for the sequential circuit shown in Fig.Q.8(b). (10 Marks)

 


Fig.Q.8(b)

- 9 a. Design and draw Mealy model of sequential detector circuit to detect the pattern 101. (10 Marks)
- b. Draw the block diagram of serial adder with accumulator and explain its working operation. (10 Marks)

- 10 a. State the guidelines for construction of state graph. (06 Marks)
- b. Draw the block diagram of binary multiplier and explain its working principle. (08 Marks)
- c. Draw and explain the operation of FPGA implementation of a parallel adder with accumulator. (06 Marks)
