 


USN

--	--	--	--	--	--	--	--	--	--



10EC45

**Fourth Semester B.E. Degree Examination, June/July 2016**  
**Fundamentals of HDL**

Time: 3 hrs.

Max. Marks: 100


**Note: Answer FIVE full questions, selecting  
at least TWO questions from each part.**

**PART – A**

- 1
  - a. Describe VHDL scalar data types with an example. (08 Marks)
  - b. Explain composite and access data types with an example for each. (08 Marks)
  - c. If A, B and C are three unsigned variables with A = 11110000, B = 01011101 and C = 0000 0000 find the value of i) A NAND B ii) A&&C iii) A ror2 iv) B<<1. (04 Marks)
  
- 2
  - a. Write a VHDL code in data flow description for a 2 bit magnitude comparator with help of truth table and simplified Boolean expressions. (12 Marks)
  - b. Write a HDL codes for 2 × 2 bit combinational array multiplier (Both VHDL and verilog). (08 Marks)
  
- 3
  - a. Write behavioral description of a half-adder in VHDL and verilog with propagation delay of 10ns. Discuss the important features of their description in VHDL and verilog. (08 Marks)
  - b. Mention the names of sequential statements associated with behavioral description. (02 Marks)
  - c. Write VHDL code for a D latch using variable assignment statement and signal assignment statements. With simulation waveforms clearly distinguish between the two statements. (10 Marks)
  
- 4
  - a. Explain with suitable examples, how binding is achieved in VHDL between.
    - i) Entity and architecture
    - ii) Entity and component
    - iii) Library and module. (06 Marks)
  - b. Write a structural description using VHDL to implement a 2:1 multiplexer with active low enable. (10 Marks)
  - c. Explain the use of generate statement. Write down format for it both in VHDL and verilog. (04 Marks)

 **PART – B**

- 5
  - a. Explain the following syntax with examples: i) Procedure; ii) Task; iii) Function. (06 Marks)
  - b. Write verilog description to convert signed binary to the integer using task. (08 Marks)
  - c. Write a VHDL function to find the greater of two signed numbers. (06 Marks)
  
- 6
  - a. Describe procedure for invoking a VHDL entity from a verilog module and a verilog module from a VHDL module. (08 Marks)
  - b. Develop mixed-language description of a 9 bit adder. (08 Marks)
  - c. Write note on VHDL packages. (04 Marks)



- 7 a. What is the necessity of mixed type description? (04 Marks)
- b. Describe the development of HDL code for an ALU and write VHDL/verilog code for ALU shown below.

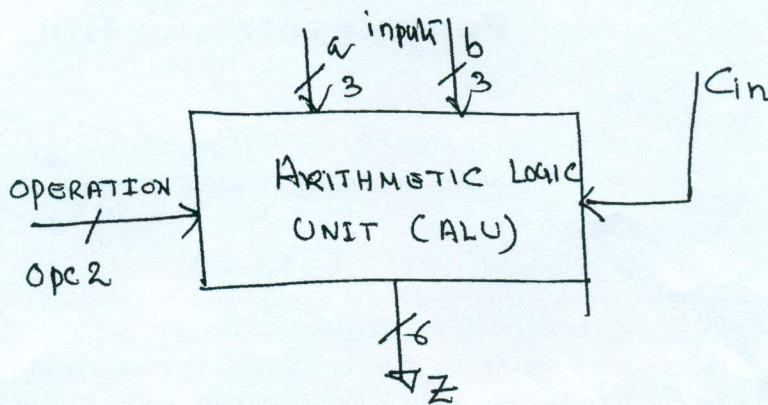


Fig.Q.7(b)

Assume the following operations: Addition, multiplication, division, no operation. (16 Marks)

- 8 a. What is synthesis? List the general steps involved in synthesis. (08 Marks)
- b. Write VHDL code for signal assignment statement  $Y = 2 * x + 3$ . Show the synthesized logic symbol and gate level diagram. Write structural code in verilog using gate level diagram. (12 Marks)

\*\*\*\*\*

Highly confidential document EDC