

Fourth Semester B.E. Degree Examination, Dec.2015/Jan.2016
Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer any FIVE full questions, selecting atleast TWO questions from each part.**
2. Missing data, if any, may be assumed suitably.

PART - A

- 1
 - a. With a neat circuit diagram, explain the basic op-amp circuit. (06 Marks)
 - b. The non - inverting amplifier uses μA 741 op-amp with $R_1 = R_3 = 2.2K$ and $R_2 = 220 K$. Determine maximum possible output offset voltage due to :
 - i) input offset voltage of 5 mV
 - ii) input bias current of $I_{B(max)} = 500 \eta A$
 - iii) Input offset current of $I_{i(OS)} = 200 \eta A$
 - iv) iv) resistance tolerance of $\pm 10\%$. (10 Marks)
 - c. Obtain the expression for output voltage for the two input inverting summing amplifier circuit. (04 Marks)

- 2
 - a. Draw a neat circuit diagram of a capacitor coupled voltage follower and explain its operation with necessary design steps. (08 Marks)
 - b. Design a high impedance capacitor - coupled non-inverting amplifier to have a low cutoff frequency of 200 Hz. The input and output voltages are to be 16 mV and 4V respectively and minimum load resistance is 10 K Ω . Select $R_2 = 1 M\Omega$ and $C_1 = 0.1 \mu F$. (06 Marks)
 - c. Explain how the upper cutoff frequency can be set for inverting amplifier with the help of neat circuit diagram and also explain design steps. (06 Marks)

- 3
 - a. Define loop gain, loop phase shift, pole frequency and phase margin. (04 Marks)
 - b. Explain miller effect compensation. (06 Marks)
 - c. For the circuit shown in Fig. Q3(c), calculate :
 - i) Full power bandwidth of 1 V peak input and op-amp slew rate of 250 V/ μs
 - ii) Maximum peak output voltage obtain for input signal of 100 KHz and with slew rate of 0.5 V/ μs . (04 Marks)

 


Fig.Q3(c)

- d. List the precautions to be observed for op-amp circuit stability. (06 Marks)



- 4 a. Design the current source circuit shown in Fig. Q4(a) to produce a 100mA output to a 40 Ω load. Use a $\pm 12V$ supply and an LM 108 op-amp. (06 Marks)

 


Fig. Q4(a)

- b. Sketch the circuit of a current amplifier with floating load. Explain circuit operation and derive an equation for current gain. (06 Marks)
- c. What are the advantages of precision rectifier over ordinary rectifier? Explain the working of a full wave precision rectifier. (08 Marks)

PART - B

- 5 a. With relevant diagram, explain the operation of negative clamper circuit using op-amp. (06 Marks)
- b. Design a triangular waveform generator to produce a $\pm 2V$, 1 KHz output. Use a $\pm 15V$ supply. Also calculate the minimum op-amp slew rate. (08 Marks)
- c. Explain the working of phase shift oscillator using op-amp. (06 Marks)
- 6 a. With relevant diagrams, explain basic inverting and non-inverting comparator circuit with $V_{ref} = 0V$. (06 Marks)
- b. With a neat circuit diagram, explain the operation of inverting Schmitt trigger circuit and discuss the design procedure. (10 Marks)
- c. Using 741 op-amp, design the first-order active low-pass filter to have a cutoff frequency of 1.2 KHz. (04 Marks)
- 7 a. Briefly explain the standard representation of 78XX series 3-terminal IC regulators and enumerate the characteristics of this type of regulators. (08 Marks)
- b. With the help of neat diagram, explain the operation of adjustable regulator using fixed 3-terminal regulator. (06 Marks)
- c. Explain the operation of basic high voltage regulator using IC 723. (06 Marks)
- 8 a. Explain the operation of a mono-stable multivibrator using 555 IC timers. (06 Marks)
- b. Explain the operation of phase-locked loop (PLL) with the help of neat block schematic diagram. (08 Marks)
- c. What output voltage would be produced by DAC whose output range is 0 to 10 V and whose input binary number is
- 10 (2 bit DAC)
 - 0110 (4 bit DAC)
 - 10111100 (for 8 bit DAC).
- (06 Marks)
