



USN

--	--	--	--	--	--	--	--	--	--

10EC46

Fourth Semester B.E. Degree Examination, Dec.2016/Jan.2017
Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
2. Use of standard resistor value and standard capacitor value table is allowed.

PART – A

- 1 a. Define the following terms with respect to opamp and specify their typical values for a 741 opamp:
i) CMRR ii) PSRR iii) Slew Rate. (06 Marks)
- b. Derive an expression for the output voltage of non-inverting summing circuit. (07 Marks)
- c. The difference of two input signals is to be amplified by a factor of 37. Each input has an amplitude of approximately 50 mV. Using LF353 opamp, design a difference amplifier to obtain approximately equal input resistance at the two input terminals and also provide common mode nulling. (07 Marks)

- 2 a. Using a BIFET opamp, design a capacitor coupled inverting amplifier with an input signal of 30 mV, a load resistance of 2.2 k Ω , $A_V = 150$ and $f_1 = 80$ Hz. (05 Marks)
- b. A high input impedance capacitor coupled non-inverting amplifier is to be designed using 741 opamp with $A_V = 120$, $f_1 = 100$ Hz, input signal of 50 mV, and the load resistance ranging from 2.7 k Ω to 27 k Ω . (09 Marks)
- c. Using 741 opamp with maximum input bias current of 500 nA, design a capacitor coupled voltage follower with a lower cutoff frequency of 120 Hz, and load resistance of 8.2 k Ω using +30V power supply. (06 Marks)

- 3 a. Discuss about the conditions that have to be fulfilled for an opamp circuit to oscillate. (05 Marks)
- b. With the help of circuit schematic and frequency response, explain how phase lag compensation can be used to stabilize opamp circuit. (05 Marks)
- c. Mention the need for Z_{in} MOD compensation. Discuss the role of compensating components in Z_{in} MOD compensation for an inverting amplifier. (05 Marks)
- d. List the precautions to be observed for opamp circuit stability. (05 Marks)

- 4 a. Design a low resistance voltage source (with reference voltage derived from potential divider) to provide an output voltage of 8V. A 741 opamp with a $\pm 15V$ supply is to be used, and the maximum output current is to be 60 mA. (08 Marks)
- b. Determine the range of resistance of externally connected resistor R_G for a LH0036 IC instrumentation amplifier to give a voltage gain adjustable from 30 to 300. (03 Marks)
- c. Design a precision full wave rectifier consisting of a summing circuit and a precision half wave rectifier to produce a 2V peak output from a sine wave input with peak value of 0.5 V and frequency of 1 MHz. Use bipolar opamps with a supply voltage of $\pm 15V$. (09 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.



10EC46

PART – B

- 5 a. A $\pm 5V$, 10 kHz square wave from a signal source with a resistance of 100Ω is to have its positive peak clamped precisely at ground level. Tilt on the output is not to exceed 1% of the peak amplitude of the wave. Design the precision clamping circuit using a supply of $\pm 12V$. (08 Marks)
- b. Draw the fundamental circuit of logarithmic amplifier and derive an expression for output voltage. (06 Marks)
- c. Design a wein bridge oscillator to have an output frequency of 15 kHz using a BIFET opamp with a supply voltage of $\pm 12V$. (06 Marks)
- 6 a. With a neat circuit diagram and associated waveforms explain the working principle of inverting Schmitt trigger circuit. (05 Marks)
- b. Explain the working principle of astable multivibrator with a neat circuit schematic and waveforms. Specify the design procedure for this circuit. (09 Marks)
- c. Using a 741 opamp, design a second order low pass filter with a cutoff frequency of 1 kHz. (06 Marks)
- 7 a. Discuss about the important characteristics of three terminal IC regulator. (04 Marks)
- b. Draw the functional block diagram of IC723 voltage regulator and explain. (06 Marks)
- c. With the help of circuit schematic explain the principle of operation of switched mode power supply. Mention its advantages. (10 Marks)
- 8 a. Draw the circuit diagram of monostable multivibrator using IC 555 and derive the expression for output pulse width. (05 Marks)
- b. Give the basic block schematic of PLL and explain the function of each block. (06 Marks)
- c. Draw the functional diagram of dual slope ADC and explain its working principle. Mention its advantages and limitations. (09 Marks)

* * * * *