



10EC46

USN

--	--	--	--	--	--	--	--

## Fourth Semester B.E. Degree Examination, Dec.2018/Jan. 2019

### Linear IC's and Applications

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any FIVE full questions, selecting atleast TWO questions from each part.

#### PART - A

1. a. Explain the operation of a basic op-amp, circuit. (08 Marks)  
b. Define the following op-amp parameters and mention their typical values for op-amp 741 :  
i) CMRR ii) slew rate. (04 Marks)  
c. Using a 741 op-amp, design a non-inverting amplifier to have a voltage gain of approximately 66. The input signal amplitude is 15mV. (04 Marks)  
d. The difference of 2 input signals is to be amplified by a factor of 37. Each input has an amplitude of 50mV. Using Lf 353 Op-amp design a suitable circuit. (04 Marks)
  
2. a. Sketch the circuit of a high Zin capacitor coupled voltage follower. Briefly explain its operation and also show that the input impedance is very high compared to the capacitor coupled voltage follower. (06 Marks)  
b. A capacitor coupled non-inverting amplifier using op-amp 741 is to have a gain of 100 and  $V_0 = 5V$ . The load resistance is  $10k\Omega$  and the lower cutoff frequency is to be 100Hz. Design a suitable circuit. (06 Marks)  
c. Design a capacitor coupled inverting amplifier to operate with a +20V supply the minimum input signal level is 50mV, the voltage gain is to be 68, the load resistance is  $500\Omega$ , and the lower cutoff frequency is to be 200Hz. Use a 741 op-amp. (08 Marks)
  
3. a. Explain the phase-lag and phase-lead frequency compensation methods briefly. (08 Marks)  
b. With the help of neat circuit diagram explain the Zin MOD method of frequency compensation. (06 Marks)  
c. Determine the upper cut-off frequency and maximum distortion free output amplitude for a voltage follower when:  
i) A 741 op-amp is used ( $f_2 = 800$  KHz and  $S = 0.5V/\mu s$ )  
ii) LF 353 op-amp is used ( $f_2 = 5MHz$ ,  $S = 13V/\mu s$ ). (06 Marks)
  
4. a. With a neat sketch, explain the working of a precision voltage source using op-amp with Zener diode. Derive an expression relating  $V_0$  and  $V_z$ . (07 Marks)  
b. Draw the circuit of an instrumentation amplifier. Explain its characteristics show how it voltage gain can be varied. (07 Marks)  
c. Using bipolar op-amps with  $V_{CC} = \pm 15V$ , design the high input impedance precision full – wave rectifier circuit. The input peak voltage is to be 1V and no amplification is to occur. Assume adequate diode current as  $500\mu A$ . (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and / or equations written eg,  $42+8 = 50$ , will be treated as malpractice.

**PART – B**

- 5 a. Briefly explain the operation of the following op-amp based applications with neat diagrams:  
 Sample and hold circuit  
 Logarithm amplifier. (08 Marks)
- b. Using 741 op-amp with a supply of  $\pm 15V$ , design a phase shift oscillator to have an output frequency of 5KHz. Assume  $C = 0.01\mu F$ . (04 Marks)
- c. With a neat circuit diagrams and waveforms briefly explain the operation of a triangular/rectangular wave generator. (08 Marks)
- 6 a. Explain the operation of an op-amp based monostable multivibrator using relevant waveforms. (08 Marks)
- b. Using a 741 op-amp with a supply of  $\pm 12V$ , design an inverting schmitt trigger circuit to have trigger points at  $\pm 3V$ . (06 Marks)
- c. Design a 2<sup>nd</sup> order low-pass filter circuit to have a cutoff frequency of 1KHz. (06 Marks)
- 7 a. With a neat functional diagram explain the operation of a low voltage regulator using IC723. (06 Marks)
- b. Discuss the performance parameters of a voltage regulator. (06 Marks)
- c. What is the principle of operation of a switched mode power supply? Discuss their advantages and disadvantages. (08 Marks)
- 8 a. With a neat circuit diagram explain the operation of a 3 bit R-2R ladder DAC. Also derive the expression for its output voltage. (06 Marks)
- b. Explain the operation of an astable multiivibrator using 555 timer with a neat functional diagram and waveforms. Derive the expression for its frequency a duty cycle. Given  $R_A = 2.2K\Omega$  and  $R_B = 6.8k\Omega$  and  $C = 0.01\mu F$ . Calculate  $T_{high}$ ,  $T_{low}$ , duty cycle and  $f_0$ . (10 Marks)
- c. Mention the applications of PLL. (04 Marks)