



USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

10EC46

Fourth Semester B.E. Degree Examination, June/July 2017

Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part. 2. Use of standard resistance and capacitance values table is permitted.

PART - A

- 1 a. With a neat circuit diagram, explain the working of a basic op-amp circuits. (07 Marks)
b. Sketch an op-amp difference amplifier circuit. Explain the operation of the circuit and derive an equation for the output voltage. (07 Marks)
c. Two signals each ranging from 0.1V to 1V are to be summed and amplified by a factor of 5. Using 741 op-amp design a suitable inverting summing amplifier circuit. (06 Marks)
2 a. Sketch and explain the operation of a capacitor coupled non-inverting amplifier circuit using single polarity power supply with necessary design steps. (08 Marks)
b. What is meant by setting upper cutoff frequency in a capacitor coupled op-amp? Explain how it is done in an inverting op-amp. (06 Marks)
c. Design a high input impedance capacitor coupled voltage follower using 741 op-amp. The lower cutoff frequency for the circuit is to be 50 Hz and the load resistance of 3.9 KΩ. Also determine the minimum theoretical input impedance of the circuit. (Consider Mmin = 50000). (06 Marks)
3 a. Explain Miller effect compensation. (08 Marks)
b. List the precautions to be observed for op-amp stability. (06 Marks)
c. Determine the upper cutoff frequency and the maximum distortion free output amplitude for a voltage follower.
i) When a 741 op-amp is used and
ii) When a LF 353 op-amp is used.
For 741: f2 = 800 kHz, s = 0.5 V/μs.
For LF353 : f2 = 5 MHz, s = 13 V/μs (06 Marks)
4 a. Draw the circuit of an instrumentation amplifier and explain its working and show how voltage gain can be varied. (08 Marks)
b. Explain the working of precision full wave rectifier using bipolar op-amp. (06 Marks)
c. Sketch the circuit of a current amplifier with floating load. Explain circuit operation and derive an equation for current gain. (06 Marks)

PART - B

- 5 a. With a neat circuit diagram and waveforms, explain the working of triangular/rectangular waveform generator. (08 Marks)
b. With a neat circuit diagram, explain multiplier and divider. (06 Marks)
c. Using a 741 op-amp with ±12 V supply, design a phase shift oscillator to have an output frequency of 5 kHz. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 6 a. With a neat circuit diagram, explain the operation of an inverting Schmitt trigger circuit. (06 Marks)
- b. Using op-amp, design a second order high pass filter to have a cutoff frequency of 7 kHz. (06 Marks)
- c. With a neat circuit diagram and waveforms, explain the operation of a stable multivibrator using op-amp. Also include design steps. (08 Marks)
- 7 a. What is an voltage regulator? With a neat sketch, explain the working of series op-amp regulator. (06 Marks)
- b. Design a voltage regulator using IC 723 to get an output voltage of 5V. (06 Marks)
- c. Explain the basic principle of operation of switching regulator. Discuss its advantages and limitations. (08 Marks)
- 8 a. Explain monostable multivibrator using IC 555. (06 Marks)
- b. Explain the operation of phase locked loop (PLL) with the help of neat block diagram. (07 Marks)
- c. With a neat block diagram, explain successive approximation ADC. (07 Marks)

* * * * *