



USN

--	--	--	--	--	--	--	--	--	--

15EC46

Fourth Semester B.E. Degree Examination, Dec.2019/Jan.2020

## Linear Integrated Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Define the following terms as applied to Op-Amp and mention their typical values for IC 741. i) CMRR ii) Slew rate iii) PSRR. (06 Marks)
- b. With a neat circuit diagram explain the basic Op-Amp circuit. (06 Marks)
- c. An operational amplifier has a specified input voltage range of  $\pm 8V$  and an output voltage range of  $\pm 14V$  when the supply voltage is  $\pm 15V$ . Calculate the maximum output voltage that can be produced i) When the Op-Amp is used as a voltage follower ii) When it is used as an amplifier with a voltage gain of 2. (04 Marks)

OR

- 2 a. With a neat circuit diagram, explain direct coupled inverting amplifier with design steps, input impedance and output impedance. (08 Marks)
- b. Derive an output voltage equation of 3 input inverting summing circuit and show how it can be converted into averaging circuit. (08 Marks)

### Module-2

- 3 a. Explain capacitor coupled voltage follower with neat circuit diagram. (08 Marks)
- b. Design a capacitor coupled non-inverting amplifier to have a voltage gain of approximately 66. The signal amplitude is to be 15mV. The load resistor is 2.2 k $\Omega$  and the lower cutoff frequency is to be 120Hz. (08 Marks)

OR

- 4 a. Explain the circuit operation of a differential input/output amplifier and derive the equation for differential voltage gain. Also show that the common mode gain is unity. (10 Marks)
- b. Design a non-saturating precision half wave rectifier to produce a 2V peak output from a sine wave input with a peak value of 0.5V and frequency of 1MHz. Use a bipolar Op-Amp with supply voltage of  $\pm 15V$ . (06 Marks)

### Module-3

- 5 a. With neat circuit diagram and waveforms, explain sample and hold circuit. (08 Marks)
- b. Explain differentiating circuit operation with neat circuit diagram and design steps. (08 Marks)

OR

- 6 a. Using 741 Op-Amp with a supply of  $\pm 12V$ , design a phase shift oscillator to have an output frequency of 3.5KHz. (06 Marks)
- b. Explain log amplifier and derive its output voltage equation. (06 Marks)
- c. Using a 741 Op-Amp with supply voltage of  $\pm 12V$ , design an inverting Schmitt trigger circuit to have trigger points of  $\pm 2V$ . (04 Marks)

**Module-4**

- 7 a. Explain the operation of second order high pass filter with a neat circuit diagram, frequency response and design steps. (08 Marks)  
b. With a neat diagram and design steps explain the operation of single stage first order bandpass filter. (08 Marks)

**OR**

- 8 a. With a neat sketch, explain the working of series Op-Amp regulator. (06 Marks)  
b. List and explain the characteristics of 3 terminal IC regulators. (04 Marks)  
c. Draw and explain functional diagram of 723 regulators. (06 Marks)

**Module-5**

- 9 a. Define the following in relation to PLL : (06 Marks)  
i) Lock in range ii) Capture range iii) Pull in time.  
b. With necessary circuit diagram, derive the equations and explain R – 2R DAC. What output voltage could be produced by a DAC whose output range is 0 to 10V and whose input binary number is i) 11(for 2 bit DAC) ii) 1011 (for 4 bit DAC). (10 Marks)

**OR**

- 10 a. Explain the operation of monostable multivibrator using 555 timer. (08 Marks)  
b. In the satable multivibrator  $R_A = 3.3k\Omega$   $R_B = 6.8k\Omega$  and  $C = 0.01 \mu F$ . Calculate : (08 Marks)  
i)  $t_{High}$  ii)  $t_{low}$  iii) free running frequency iv) duty cycle D.

\*\*\*\*\*