



--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination, June/July 2017
Linear Integrated Circuits

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. With a neat circuit diagram, explain basic operational amplifier circuit. (06 Marks)
 b. Define CMRR of an operational amplifier. A741 op-amp is used in a non-inverting amplifier with a voltage gain of 50. Calculate the typical output voltage that would result from a common mode input with a peak level of 100 mV. (05 Marks)
 c. Design an averaging circuit to give the average of two inputs which each range from 0.1 V to 1 V. Use 741 op-amp. (05 Marks)

OR

- 2 a. Sketch the circuit of an op-amp difference amplifier circuit. Discuss the working and common mode nulling capability with necessary circuit modification and equations. (08 Marks)
 b. With a neat circuit diagram, explain direct coupled voltage follower. Also compare voltage follower with emitter follower. (08 Marks)

Module-2

- 3 a. Draw the circuit of a capacitor coupled non-inverting amplifier and explain with necessary design equations. Design a high input impedance capacitor coupled non-inverting amplifier with a gain of 100 and lower cut off frequency of 100 Hz. Assume the load resistance is 2.2 K Ω and input parasitic capacitance as 15 pF. (10 Marks)
 b. Design a capacitor coupled inverting amplifier for a pass band gain of 100, lower cut off frequency of 120 Hz and upper cutoff frequency to be 5 kHz. Use LF353 BIFET opamp and assume load resistance as 2 K Ω . (06 Marks)

OR

- 4 a. Draw the circuit of an instrumentation amplifier and explain. Also show the method of nulling common mode outputs and how dc output voltage can be level shifted. (09 Marks)
 b. Design a non-saturating precision half wave rectifier to produce a 2 V peak output from a 1 MHz sine wave input with a 0.5 V peak value. Use a bipolar op-amp with a supply voltage of $\pm 15V$. (07 Marks)

Module-3

- 5 a. Sketch the circuit of a symmetrical precision clipper and explain with necessary equations and waveforms. Using bipolar opamp design the circuit to clip a 100 kHz sine wave at $\pm 3V$ level. (09 Marks)
 b. Explain the working of Weinbridge oscillator with the help of circuit diagram, waveforms and equations. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Sketch the circuit of fundamental log amplifier and explain its operation. Also derive an expression for its output voltage. Also mention its drawback. (08 Marks)
- b. With a neat circuit diagram, explain the operation of inverting Schmitt trigger. Using 741 op-amp with a supply of ± 12 V, design an inverting Schmitt trigger circuit to have trigger points of UTP = 0 V and LTP = -1 V. (08 Marks)

Module-4

- 7 a. Explain the operation of first order low pass filter with neat circuit diagram, frequency response and design steps. Using a 741 opamp, design a first order active low pass filter to have a cutoff frequency of 2 kHz. (08 Marks)
- b. Draw the circuit of a single stage band pass filter and explain the operation with necessary design equations. (08 Marks)

OR

- 8 a. Draw the standard representation of 78XX series 3-terminal IC regulator and enumerate the characteristics of this type of regulators. Also define the following performance parameters of a voltage regulator. (i) Line regulation (ii) Load regulation (iii) Ripple rejection (08 Marks)
- b. With a neat diagram, explain the operation of low voltage regulator using IC723. Design a voltage regulator circuit using LM723 to obtain $V_0 = 5$ V and $I_0 = 2$ A. (08 Marks)

Module-5

- 9 a. With a neat block schematic, explain the operating principle of PLL. Also define (i) Lock-in range (ii) Capture range and (iii) Pull-in time. (08 Marks)
- b. Explain the working of Flash ADC with necessary diagram. An 8 bit ADC outputs all 1's when $V_i = 2.55$ V. Find its (i) resolution in mV/LSB and (ii) digital output when $V_i = 1.28$ V (08 Marks)

OR

- 10 a. Draw the internal schematic of IC555, configuring it for astable operation and explain with necessary equations and waveforms. (08 Marks)
- b. With necessary circuit diagram and equations, explain R-2R DAC. What output voltage would be produced by a DAC whose output range is 0 to 10 V and whose input binary number is, (i) 1010 (for 4 bit DAC) (ii) 10111100 (for an 8 bit DAC). (08 Marks)
