

USN

--	--	--	--	--	--	--	--	--	--



10EC56

Fifth Semester B.E. Degree Examination, Dec.2015/Jan.2016

Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.
2. Assume missing data, if any.

PART – A

- 1 a. Explain with a neat diagram, enhancement mode transistor action of MOS transistor. (08 Marks)
 b. Using neat diagram, describe fabrication steps for n-MOS transistor. (08 Marks)
 c. Compare CMOS and Bipolar technologies. (04 Marks)
- 2 a. What do you mean by Lambda (λ) based design rule? Explain, indicate and draw design rule for PMOS, CMOS and n-mos. (12 Marks)
 b. Using CMOS logic draw schematic and Layout diagram for $Y = \overline{AB + CD}$. (08 Marks)
- 3 a. Explain why p-MOS and n-MOS has been used in CMOS complementary logic. Discuss CMOS complementary logic with an example. (06 Marks)
 b. Describe the following logic structures with an example.
 i) Pseudo – n-MOS logic
 ii) Dynamic CMOS logic (10 Marks)
 c. Using Bi-CMOS logic structure design a schematic circuit for $h = \overline{ab + c}$. (04 Marks)
- 4 a. What is sheet resistance? Derive the expression for sheet resistance. (08 Marks)
 b. Explain delay unit. (06 Marks)
 c. Discuss the scaling factors for n-MOS transistor. (06 Marks)

PART – B

- 5 a. Discuss the architectural issues of CMOS subsystem design. (04 Marks)
 b. Explain combinational logic using a parity generator. (08 Marks)
 c. Explain: i) Dynamic register element ii) Dynamic shift register. (08 Marks)
- 6 a. Design and explain 4bit shifter using 4×4 cross bar and barrel shifter. (12 Marks)
 b. Explain with a neat diagram 4 – bit serial – parallel multiplier. (08 Marks)
- 7 a. Explain with a neat diagram, a three transistor dynamic RAM cell. (08 Marks)
 b. Explain CMOS Pseudo – static memory cell using circuit and stick diagram. (12 Marks)
- 8 a. Discuss the floor plan and layout using 4 – bit processor. (08 Marks)
 b. Write a short note on
 i) Built – in – self – test (BIST)
 ii) Scan design technology. (12 Marks)

* * * * *

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.