

CBCS SCHEME



USN

--	--	--	--	--	--	--	--

15EC552

Fifth Semester B.E. Degree Examination, June/July 2018 Switching and Finite Automata Theory

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. What is threshold element? Write the symbol for a threshold element. (04 Marks)
- b. Explain the following:
 - (i) Magnetic-core threshold element (06 Marks)
 - (ii) Resistor-transistor threshold element. (06 Marks)
- c. Explain the capabilities and limitations of threshold logic. (06 Marks)

OR

- 2 a. Find the function $f(x_1, x_2, x_3, x_4)$ realized by each of the threshold networks shown in Fig.Q2(a). Show the map of each function. (10 Marks)

 


Fig.Q2(a)

- b. Explain the following :
 - (i) Unate functions (06 Marks)
 - (ii) Linear Separability. (06 Marks)

Module-2

- 3 a. What is a Static Hazard? Design a hazard-free switching circuit for a function $T(x, y, z) = \Sigma(1, 3, 4, 5)$ (06 Marks)
- b. Explain the following :
 - (i) Preset Experiment (10 Marks)
 - (ii) Adaptive Experiment (10 Marks)

OR

- 4 a. What is a Boolean difference? Explain the properties of Boolean differences. (10 Marks)
- b. Write the fault table for derivation of minimal set of fault-detection test for the following circuit shown in Fig.Q4(b) (06 Marks)

 


Fig.Q4(b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.



Module-3

- 5 a. What are sequential machines? Explain finite state model and its mathematical representations. (06 Marks)
 b. What is merger graph? Draw the merger graph for the incompletely specified machine M_1 shown in table Q5(b). (10 Marks)

Machine M_1

PS	NS, Z			
	I_1	I_2	I_3	I_4
A	-	C, 1	E, 1	B, 1
B	E, 0	-	-	-
C	F, 0	F, 1	-	-
D	-	-	B, 1	-
E	-	F, 0	A, 0	D, 1
F	C, 0	-	B, 0	C, 1

Table Q5(b)

OR

- 6 a. Explain the following :
 (i) Mealy machine (ii) Moore machine. (06 Marks)
 b. Draw the merger table for the incompletely specified machine M_2 shown in table Q6(b) and draw the compatibility graph for machine M_2 . (10 Marks)

Machine M_2

PS	NS, Z	
	I_1	I_2
A	E, 0	B, 0
B	F, 0	A, 0
C	E, -	C, 0
D	F, 1	D, 0
E	C, 1	C, 0
F	D, -	B, 0

Table Q6(b)

Module-4

- 7 a. Given the machine table in Table Q7(a) M_3 and two assignments α and β , derive in each case the logical equations for the state variables and draw the circuit diagrams of assignments α and β . (10 Marks)

Machine M_3

PS	NS		Z	
	$x=0$	$x=1$	$x=0$	$x=1$
A	A	D	0	1
B	A	C	0	0
C	C	B	0	0
D	C	A	0	1

Table Q7(a)

	y_1	y_2		y_1	y_2
A \rightarrow	0	0	A \rightarrow	0	0
B \rightarrow	0	1	B \rightarrow	0	1
C \rightarrow	1	1	C \rightarrow	1	0
D \rightarrow	1	0	D \rightarrow	1	1

Assignment α

Assignment β

- b. Explain the following :
 (i) Output - consistent partition
 (ii) Input - consistent partition
 (iii) Autonomous clock.

(06 Marks)