



USN

--	--	--	--	--	--	--	--	--	--

10EC63

Sixth Semester B.E. Degree Examination, Dec.2016/Jan.2017
Micro Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Define the following parameters with respect to MOSFET:
 - i) Threshold voltage; ii) Overdrive voltage. (05 Marks)
- b. Explain the breakdown effect occurs in MOSFET. (05 Marks)
- c. Draw the biasing circuit using a drain to gate feedback resistor and explain it. (05 Marks)
- d. For the circuit shown in Fig.Q.1(d), find the values of R and V_D to obtain a current I_D of $80\mu A$. Let the NMOS transistor have $V_t = 0.6V$, $\mu_n C_{ox} = 200 \mu A/V^2$, $L = 0.8 \mu m$ and $W = 4 \mu m$. Assume $\lambda = 0$. (05 Marks)

 


Fig.Q.1(d)

- 2 a. What are the disadvantages due to short-channel effects? (05 Marks)
- b. The high frequency response of an amplifier is characterized by the TF

$$F_H(s) = \frac{1 - \frac{s}{10^5}}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{4 \times 10^4}\right)}$$
 Determine the 3-dB frequency. (05 Marks)
- c. What is current steering? Mention its advantages. (05 Marks)
- d. Draw the circuit of basic MOSFET current source and explain it. (05 Marks)
- 3 a. Draw the circuit and small signal equivalent circuit of common source amplifier with active load and explain it. (06 Marks)
- b. What is cascade amplifier and mention the basic idea behind the cascade amplifier? (06 Marks)
- c. Draw the circuit of double cascading and explain it. (08 Marks)
- 4 a. Draw the transistor pairing circuits and mention the advantages of each pair. (06 Marks)
- b. Draw the circuit of cascade MOS current mirror and explain it. (06 Marks)
- c. Explain the operation of a MOS differential pair with a common mode input voltage and mention the relevant equations. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.



PART – B

- 5 a. The differential amplifier shown in Fig.Q.5(a) uses transistors with $\beta = 100$. Evaluate:
- Input differential resistance (R_{id}).
 - Overall differential voltage gain V_o/V_{sig} (neglect the effect of V_o).
 - CMRR in dB. (Assume $A_{cm} = 5 \times 10^{-4}$).
 - Input common mode resistance (assuming that the early voltage $V_A = 100V$). (10 Marks)

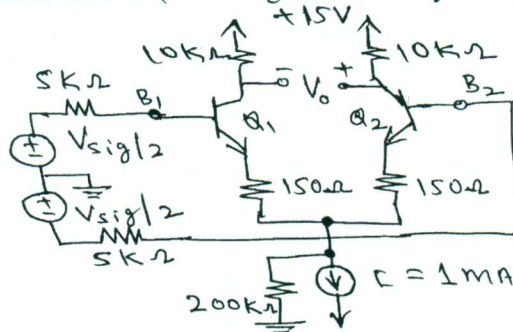


Fig.Q.5(a)

- b. Draw the two-stage CMOS Op-Amp circuit and explain it. (10 Marks)
- 6 a. Explain the properties of negative feedback. (10 Marks)
- b. Explain the effect of feedback on the amplifier stability and pole location. (07 Marks)
- c. What are the properties of current amplifier? (03 Marks)
- 7 a. Derive the expression for the closed loop gain V_o/V_{in} of the circuit shown in Fig.Q.7(a). (08 Marks)

 


Fig.Q.7(a)

- b. With the help of mathematical analysis, explain how to minimize the temperature effect in logarithmic amplifier. (10 Marks)
- c. What are DC imperfections? (02 Marks)
- 8 a. Obtain the PUN from the PDN and vice versa for the following expressions: (12 Marks)
- $Y = \overline{A(B + CD)}$
 - $Y = \overline{\overline{A}(B + AC)}$
- b. Define the following parameters with respect to CMOS: (08 Marks)
- Propagation delay
 - Robustness
 - Delay power product
 - Dynamic power dissipation.
