

**Sixth Semester B.E. Degree Examination, Dec.2018/Jan.2019**  
**Microelectronics Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
atleast THREE questions from Part-A and TWO from Part-B.**

**PART - A**

- 1 a. Draw the physical structure and hence explain the operation of NMOS enhancement type transistor. (06 Marks)
  - b. Derive the expression for drain current  $i_D$  in triode and saturation region. (06 Marks)
  - c. Consider a CMOS process for which  $L_{\min} = 0.8 \mu\text{m}$ ,  $t_{\text{ox}} = 15 \text{ nm}$ ,  $\mu_n = 550 \text{ cm}^2/\text{V-s}$  and  $V_t = 0.7 \text{ V}$ .
    - (i) Find  $C_{\text{ox}}$  and  $K'_n$
    - (ii) For an NMOS transistor with  $\frac{W}{L} = \frac{16 \mu\text{m}}{8 \mu\text{m}}$ , calculate the values of  $V_{\text{OV}}$ ,  $V_{\text{GS}}$  and  $V_{\text{DSmin}}$  needed to operate the transistor in the saturation region with a DC current  $I_D = 100 \mu\text{A}$ .
    - (iii) For the device in (ii), find the value of  $V_{\text{OV}}$  and  $V_{\text{GS}}$  required to cause the device to operate as a  $1000 \Omega$  resistor for a very small  $V_{\text{DS}}$ . (08 Marks)
- 2 a. The NMOS and PMOS transistors in the circuit of Fig.Q2(a) are matched with  $K'_n \left( \frac{W_n}{L_n} \right) = K'_p \left( \frac{W_p}{L_p} \right) = 1 \text{ mA/V}^2$  and  $V_{\text{tn}} = -V_{\text{tp}} = 1 \text{ V}$ . Assuming  $\lambda = 0$  for both devices, find the drain currents  $i_{\text{DN}}$  and  $i_{\text{DP}}$  and the voltage  $V_0$  for  $V_1 = 0 \text{ V}, +2.5 \text{ V}, -2.5 \text{ V}$ .

 


Fig.Q2(a)

- b. Draw the circuit diagram of source follower amplifier. Draw its small signal equivalent circuit with  $r_0$ . Obtain the expression for  $V_0$ ,  $A_V$ ,  $A_{V_0}$ ,  $G_V$  and  $R_{\text{out}}$ . (10 Marks)
  - c. State and prove Miller's theorem. (04 Marks)
- 3 a. Draw the MOSFET constant current source circuit and explain its operation. (04 Marks)

- b. Given  $V_{DD} = 3V$  and using  $I_{REF} = 100 \mu A$ , it is required to design MOSFET constant current source shown in Fig.Q3(b) to obtain an output current whose nominal value is  $100 \mu A$ . Find  $R$  if  $Q_1$  and  $Q_2$  are matched and have channel lengths of  $1 \mu m$ , channel widths of  $10 \mu m$ ,  $V_t = 0.7V$ , and  $K'_n = 200 \mu A/V^2$ . What is the lowest possible value of  $V_0$ ? Assuming that for this process technology the early voltage  $V_A = 20 V/\mu m$ , find the output resistance of the current source. Also, find the change in output current resulting from a  $+1V$  change in  $V_0$ .

 


Fig.Q3(b)

(08 Marks)

- c. Explain the operation of a MOS current steering circuit and mention its advantages.

(08 Marks)

- 4 a. A CMOS common source amplifier shown in Fig.Q4(a) is fabricated in a  $0.18 \mu m$  technology has  $\frac{W}{L} = \frac{7.2 \mu m}{0.36 \mu m}$  for all transistors,  $K'_n = 387 \mu A/V^2$ ,  $K'_p = 86 \mu A/V^2$ ,  $I_{REF} = 100 \mu A$ ,  $V_{An} = 5 V/\mu m$  and  $|V_{Ap}| = 6 V/\mu m$ .  $g_m$ ,  $r_{o1}$ ,  $r_{o2}$  and the voltage gain.

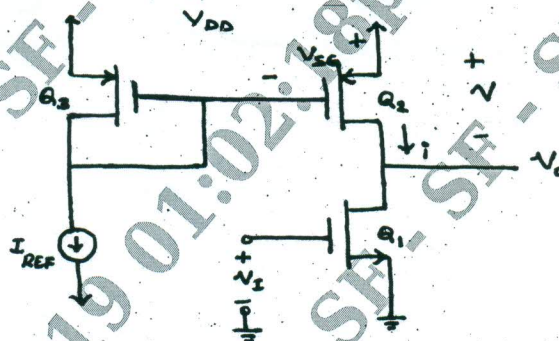


Fig.Q4(a)

(10 Marks)

- b. For the high frequency equivalent circuit for a common source MOSFET amplifier shown in Fig.Q4(b). Derive an expression for 3-dB frequency,  $f_H$  using Miller's theorem and open circuit time constant.

(10 Marks)

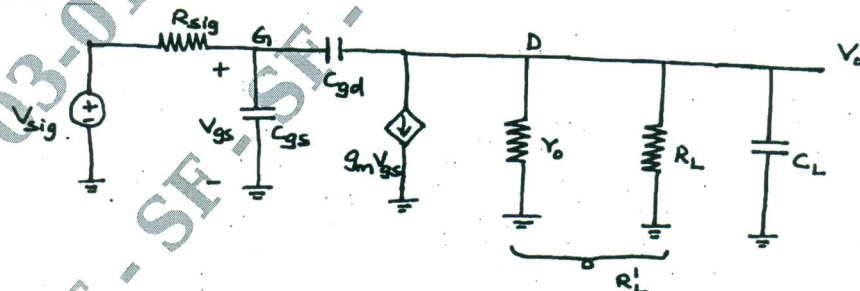


Fig.Q4(b)

- 5 a. Explain the operation of MOS differential pair with a common mode input voltage. (04 Marks)
- b. A MOS differential pair is operated at a total bias current of 0.8 mA, using transistors with a W/L ratio of 100,  $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$ ,  $V_A = 20\text{V}$ , and  $R_D = 5 \text{ k}\Omega$ . Find  $V_{OV}$ ,  $g_m$ ,  $r_o$  and  $A_d$ . (08 Marks)
- c. With a neat circuit diagram, explain the operation of two stage CMOS operational amplifier configuration. (08 Marks)

**PART - B**

- 6 a. What are the properties of negative feedback? Explain in more detail. (06 Marks)
- b. Explain the effect of feedback on the amplifier poles. (06 Marks)
- c. Discuss the method of frequency compensation for modifying open-loop gain  $A(s)$  so that the closed loop amplifier is stable, by introducing a new pole in transfer function at sufficiently low frequency. (08 Marks)
- 7 a. Design an inverting op-amp circuit to form the weighted sum  $V_0$  of two inputs  $V_1$  and  $V_2$ . It is required that  $V_0 = -(V_1 + 5V_2)$ . Choose values for  $R_1$ ,  $R_2$  and  $R_f$  so that for a maximum output of 10 V the current in the feedback resistor will not exceed 1 mA. (04 Marks)
- b. Explain in detail dc imperfections of an operational amplifier. (06 Marks)
- c. An op-amp wired in the inverting configuration with the input grounded, having  $R_2 = 100\text{k}\Omega$  and  $R_1 = 1 \text{ k}\Omega$  has an output DC voltage of  $-0.3\text{V}$ . If the input bias current is known to be very small, find the input offset voltage. (04 Marks)
- d. Explain how to minimize the temperature effect in a logarithmic amplifier. (06 Marks)
- 8 a. Explain in detail the static and dynamic operation of a CMOS inverter. (08 Marks)
- b. Sketch a CMOS realization for the function  $Y = A + B(C + D)$  (04 Marks)
- c. Provide transistor  $\frac{W}{L}$  ratios for the logic circuit shown in Fig.Q8(c). Assume that for the basic inverter  $n = 1.5$  and  $p = 5$  and that the channel length is  $0.25 \mu\text{m}$ . (08 Marks)

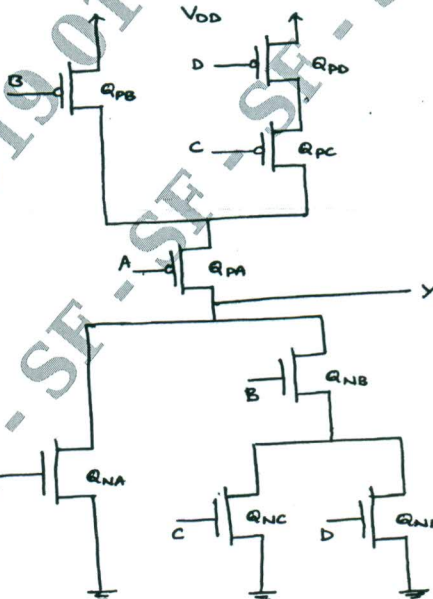


Fig.Q8(c)

\*\*\*\*\*