

USN

--	--	--	--	--	--	--	--	--	--

15EC655

Sixth Semester B.E. Degree Examination, Feb./Mar. 2022 Microelectronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain channel length modulation. Obtain the modified equation of drain current in saturation region operation of MOSFET. (07 Marks)
- b. Write a note on body and temperature effects observed in MOSFETs. (05 Marks)
- c. An enhancement PMOS transistor has $K_p^1(W/L) = 80\mu A/V^2$, $V_t = -1.5V$ and $\lambda = -0.02V^{-1}$. The gate is connected to ground and the source to +5V. Find the drain current for $V_D = +4V$. (04 Marks)

OR

- 2 a. For the common source circuit shown in Fig.Q.2(a), sketch the transfer characteristic and obtain analytical expressions for the same. (08 Marks)

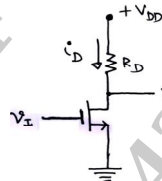


Fig.Q.2(a)

- b. An n-channel enhancement MOSFET is measured to have a drain current of 4mA at $V_{GS} = V_{DS} = 5V$ and of 1mA at $V_{GS} = V_{DS} = 3V$. What are the values of $K_n^1(W/L)$ and V_t for this device? (04 Marks)
- c. For the circuit shown in Fig.Q.2(c), what should be the value of R_D to establish a drain voltage of 0.1V? What is the effective resistance between drain and source at this operating point? Let $V_t = 1V$ and $K_n^1(W/L) = 1mA/V^2$. (04 Marks)

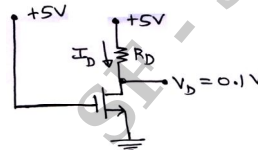


Fig.Q.2(c)

Module-2

- 3 a. Consider the MOSFET circuit shown in Fig.Q.3(a). Derive an expression for MOSFET trans conductance parameter, g_m . Also, show how g_m can be obtained from the transfer characteristic of the device. (06 Marks)

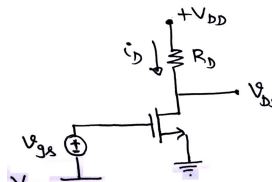


Fig.Q.3(a)

- b. Derive the expression of higher cut-off frequency for a common source amplifier circuit. (08 Marks)
- c. In a MOS amplifier circuit, for a particular value of I_D (DC bias current), the value device g_m is found to be 0.75mA/V . If I_D is increased by 4 times, what will be the new value of device g_m . (02 Marks)

OR

- 4 a. Design the biasing circuit shown in Fig.Q.4(a) to establish a drain current, $I_D = 0.5\text{mA}$. The MOSFET has $V_t = 1\text{V}$, $K_n^1 \left(\frac{W}{L}\right) = 1\text{mA/V}^2$ and $V_{DD} = 15\text{V}$. Assume one-third of V_{DD} across R_D and R_S , and neglect channel length modulation, $\lambda = 0$. Determine percentage change in value of I_D when MOSFET is replaced by another having $V_t = 1.5\text{V}$. (09 Marks)

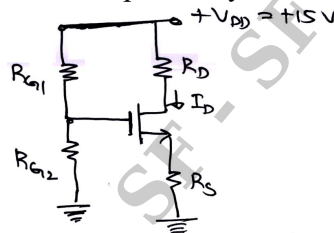


Fig.Q.4(a)

- b. Obtain T-model for a MOSFET from its hybrid-II model. (04 Marks)
- c. For an n-channel MOSFET with $t_{ox} = 10\text{nm}$, $L = 1\mu\text{m}$, $W = 10\mu\text{m}$, $L_{ov} = 0.05\pi\text{m}$ and $C_{sbo} = C_{dbo} = 10\text{fF}$. Find the values of C_{ox} , C_{ov} and C_{gs} . Note that permittivity of oxide, $\epsilon_{ox} = 3.9\epsilon_0$. (03 Marks)

Module-3

- 5 a. Consider a source follower circuit. Let $R_{sig} = 1\text{M}\Omega$, $R_L = 15\text{K}\Omega$, $R_G = 4.7\text{M}\Omega$, $g_m = 1\text{m}\Omega$ and $r_o = 150\text{K}\Omega$. Find R_{in} , A_V , R_{out} and G_V of the circuit. (06 Marks)
- b. Explain MOSFET current steering circuit. (07 Marks)
 - c. Mention the effects of using source resistance, R_S , in a common source amplifier circuit. (03 Marks)

OR

- 6 a. Derive the approximate expression for upper cut off frequency (3dB) for the direct coupled IC amplifier in the case of absence of dominant pole. (06 Marks)
- b. Compare BJT and MOSFET with respect to transconductance, g_m and output resistance, r_o . (04 Marks)
 - c. Obtain the value of R in the circuit of Fig.Q.6(c) for $V_{DD} = 3\text{V}$ and $I_{REF} = I_o = 100\mu\text{A}$. Let Q_1 and Q_2 be matched, channel lengths = $1\mu\text{m}$, channel widths = $10\mu\text{m}$, $V_t = 0.7\text{V}$ and $K_n^1 = 200\mu\text{A/V}^2$. Assuming early voltage parameter, $V_A^1 = 20\text{V}/\mu\text{m}$, find the output resistance of the circuit. Also, find the lowest possible value of V_o . (06 Marks)

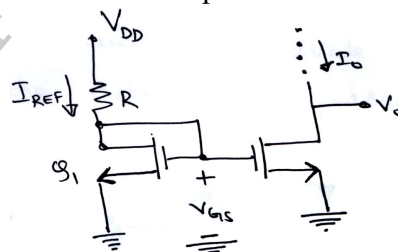


Fig.Q.6(c)

