

USN

--	--	--	--	--	--	--	--	--	--

15EC655

Sixth Semester B.E. Degree Examination, July/August 2021 Microelectronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions.

- 1 a. Derive an expression of drain current in NMOS transistor for triode and saturation regions, with necessary diagrams. (08 Marks)
- b. Design the circuit shown in Fig.Q1(b) to obtain a current I_D of $80 \mu\text{A}$. Find the value required for R and find the dc voltage V_D . Let the NMOS transistor have $V_t = 0.6 \text{ V}$, $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $L = 0.8 \mu\text{m}$ and $w = 4 \mu\text{m}$. Neglect the channel-length modulation effect (i.e. assume $\lambda = 0$).

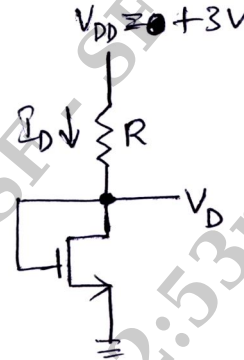


Fig.Q1(b)

- c. Explain the effect of substrate bias on threshold voltage of MOS transistors. (04 Marks)
- 2 a. With a neat diagram, explain the operation of enhancement-type NMOS transistor in detail. (08 Marks)
- b. An NMOS transistor is fabricated in a $0.4 \mu\text{m}$ process having $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ and $V'_A = 50 \text{ V}/\mu\text{m}$ of channel length. If $L = 0.8 \mu\text{m}$ and $W = 16 \mu\text{m}$, find V_A and λ . Find the value of I_D that results when the device is operated with an overdrive voltage $V_{OV} = 0.5 \text{ V}$ and $V_{DS} = 1 \text{ V}$. Also find the value of r_0 at this operating point. If V_{DS} is increased by 2 V , what is the corresponding change in I_D ? (08 Marks)
- 3 a. With a neat diagram, explain the operation of the common-source amplifier. Also derive the expressions for input and output resistance and voltage gain. (10 Marks)
- b. Explain briefly the MOSFET internal capacitances. (06 Marks)
- 4 a. Explain the biasing of MOSFET using constant current source. (06 Marks)
- b. Explain the small signal model of MOSFET and how the T-equivalent circuit model can be obtained. (06 Marks)
- c. A MOSFET is to operate at $I_D = 0.1 \text{ mA}$ and is to have $g_m = 1 \text{ mA}/\text{V}$. If $K'_n = 50 \mu\text{A}/\text{V}^2$, find the required (W/L) ratio and the overdrive voltage. (04 Marks)
- 5 a. Compare the following characteristics of MOSFET and BJT:
 - (i) Transconductance g_m
 - (ii) Intrinsic gain A_o(04 Marks)

- b. Given $V_{DD} = 3V$ and using $I_{Ref} = 100 \mu A$, it is required to design the circuit of Fig.Q5(b) to obtain an output current whose nominal value is $100 \mu A$. Find R if Q_1 and Q_2 are matched and have channel lengths of $1 \mu m$, channel widths of $10 \mu m$, $V_t = 0.7 V$, and $K'_n = 200 \mu A/V^2$. What is the lowest possible value of V_0 ? Assuming that for this process technology the early voltage $V'_A = 20 V/\mu m$, find the output resistance of the current source. Also, find the change in output current resulting from a $+1V$ change in V_0 .

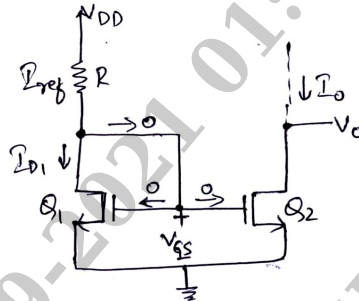


Fig.Q5(b) **(06 Marks)**

- c. Derive the expression for determining the 3-dB frequency (ω_H) of an amplifier. **(06 Marks)**

- 6 a. Explain briefly the operation of MOS current steering circuit. **(06 Marks)**
 b. For the circuit shown in Fig.Q6(b), find the midband voltage gain $A_m = V_0/V_{sig}$ and the upper 3-dB frequency f_H . Where $R_{sig} = 100 K\Omega$, $R_{in} = 420 K\Omega$, $C_{gs} = C_{gd} = 1 PF$, $g_m = 4 mA/V$ and $R'_L = 3.33 K\Omega$.

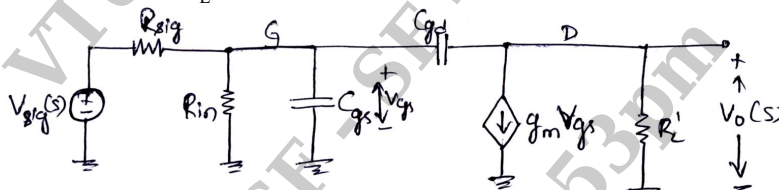


Fig.Q6(b) **(06 Marks)**

- c. The high frequency response of an amplifier is characterized by the transfer function.

$$F_H(s) = \frac{1 - \frac{s}{10^5}}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{4} * 10^4\right)}$$

Determine the 3-dB frequency approximately and exactly. **(04 Marks)**

- 7 a. Explain the high frequency response of the CS amplifier and analyze using Miller's theorem. **(08 Marks)**
 b. Consider a common-gate amplifier specified as follows:
 $W/L = 7.2 \mu m/0.36 \mu m$, $K'_n = 387 \mu A/V^2$, $r_0 = 18 K\Omega$, $I_D = 100 \mu A$, $g_m = 1.25 mA/V$, $x = 0.2$, $R_S = 10 K\Omega$, $R_L = 100 K\Omega$, $C_{gs} = 20 fF$, $C_{gd} = 5 fF$ and $C_L = 0$. Find A_{V_0} , R_{in} , R_{out} , G_v , G_{is} , G_i and f_H . **(08 Marks)**
- 8 a. Explain the operation of MOS cascode amplifier. **(08 Marks)**
 b. Explain the effect of source resistance on transconductance and voltage gain of a CS amplifier. **(08 Marks)**
- 9 a. Explain the operation of MOS differential pair with a common mode input voltage. **(08 Marks)**
 b. Explain the effect of g_m mismatch on CMRR of a MOS differential amplifier. **(08 Marks)**
- 10 a. With a neat diagram, explain the operation of a two-stage CMOS op-amp. **(08 Marks)**
 b. Obtain the expression for differential gain of the active-loaded MOS pair. **(08 Marks)**
