

# CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

18EC644

## Sixth Semester B.E. Degree Examination, July/August 2022 Digital System Design using Verilog

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Develop a verilog model for a 4:1 multiplexer. (04 Marks)
- b. Explain with illustration, a simple design methodology followed in IC industries. (08 Marks)
- c. Develop verilog model for a 7-segment decoder, include an additional input, blank that overrides the BCD input and causes all segments not to be lit. (08 Marks)

OR

- 2 a. With a neat block diagram, explain a design methodology for hardware/software co-design. (10 Marks)
- b. Develop a verilog model of the priority encoder for use in a domestic burglar alarm that has sensors for each of eight zones. Sensor signal is '1' when an intrusion is detected in that zone and '0' otherwise. Zone 1 is having highest priority, down to zone 8 having lowest priority. (10 Marks)

### Module-2

- 3 a. Determine whether there is an error in the ECC word 000111000100 and if so correct it. (06 Marks)
- b. Design a 64K × 8 bit composite memory using four 16K × 8 bit components and also explain how memory components with tristate data outputs simplify the construction of larger memories. (08 Marks)
- c. Explain about the multiport memories. (06 Marks)

OR

- 4 a. What is the difference between asynchronous static RAM and synchronous static RAM? (08 Marks)
- b. Develop a verilog model of a dual port 4K × 16 bit flow through SSRAM. One port allows data to be written and read, while the other port allows data to be read. (08 Marks)
- c. Compute the 12-bit ECC word corresponding to the 8-bit data word '01100001'. (04 Marks)

### Module-3

- 5 a. Outline and explain the internal organization of FPGA. (10 Marks)
- b. Briefly explain programmable array logic. (10 Marks)

OR

- 6 a. Explain the concept differential signaling. How does differential signaling improve noise immunity? (10 Marks)
- b. What distinguishes a platform FPGA from a simple FPGA? (05 Marks)
- c. Explain different types of PCB design. (05 Marks)



18EC644

**Module-4**

- 7 a. With a neat diagram, explain R-string DAC and R/2R ladder DAC. (10 Marks)  
b. Explain any four serial interface standards. (10 Marks)

**OR**

- 8 a. Explain any four analog sensors. (10 Marks)  
b. Explain flash ADC and successive approximation ADC with the help of necessary diagrams. (10 Marks)

**Module-5**

- 9 a. Explain briefly area, power and timing optimization in digital circuits. (10 Marks)  
b. Explain fault model and fault simulation. (10 Marks)

**OR**

- 10 a. Demonstrate Built-In Self Test (BIST) techniques. (10 Marks)  
b. Explain the hardware and software co-design flow. (10 Marks)

\* \* \* \* \*