

--	--	--	--	--	--	--	--	--	--

Seventh Semester B.E. Degree Examination, July/August 2022
Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1
 - a. Mention any four properties of a super power device should posses. (02 Marks)
 - b. Explain any four different types of power converter circuit with the help of circuit diagram, input and output waveforms. Also mention one application of each type. (10 Marks)
 - c. With the circuit diagram, input and output waveforms, explain the control characteristics of SCR and IGBT. (08 Marks)
- 2
 - a. What is the necessity of Base Drive Control in a power transistor? Explain proportional base control. (06 Marks)
 - b. Draw the equivalent model of BJT and explain the switching characteristics of power transistor. (08 Marks)
 - c. A transistor switch of Fig Q2(c) has β in the rang of 8 to 40. Calculate :
 - i) the value of R_B that results in saturation, with an overdrive factor of 5
 - ii) the forced β_f and
 - iii) the power loss in the transistor.

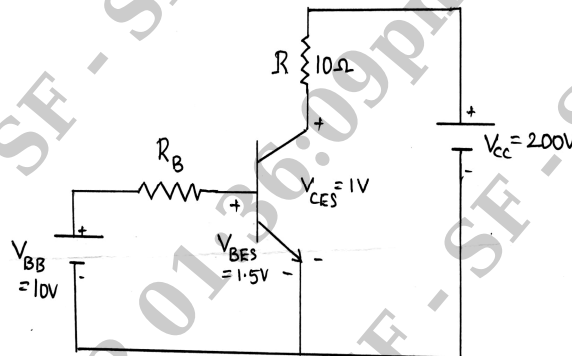


Fig Q2(c)

- 3
 - a. Explain the two transistor model of SCR and derive the formula. (10 Marks)
 - b. Explain the dynamic characteristics of SCR during turn off with suitable waveforms. (06 Marks)
 - c. Design the snubber circuit elements R_s and C_s connected across the SCR, given that $\frac{dv}{dt}(\max) = 18\text{V}/\mu\text{s}$ and $\frac{di}{dt}(\max) = 45\text{A}/\mu\text{s}$. An inductor $L = 0.1\text{H}$ and a resistance $R \ll R_s$ are in series with the SCR with a 300V, DC applied to the circuit. (04 Marks)
- 4
 - a. With a circuit diagram and waveform, explain the working of a single phase semicontrolled Rectifier. Derive an expression for the average voltage across the R-L load. (10 Marks)
 - b. A single phase full converter is operated from a 120V, 60Hz supply. The load current with an average of I_a is continuous with negligible ripple current. If the delay angle is $\alpha = \frac{\pi}{3}$, calculate : i) Harmonic factor ii) Displacement factor iii) Power factor. (06 Marks)
 - c. What are the advantages of I- ϕ dual converter operation with circulating current? (04 Marks)

PART – B

- 5 a. Explain or compare natural and forced commutation. (04 Marks)
 b. With the help of circuit diagram and waveforms explain the operation of self commutation. (10 Marks)
 c. An AC voltage controller in Fig Q5(c), has a resistive load of $R = 10\Omega$ and the root mean-square input voltage is $V_s = 120V$, 60Hz. The thyristor switch is ON for $n = 25$ cycles and is OFF for $m = 75$ cycles. Determine: i) The rms output voltage V_o ii) input power factor (PF) and iii) The average and rms current of thyristors.


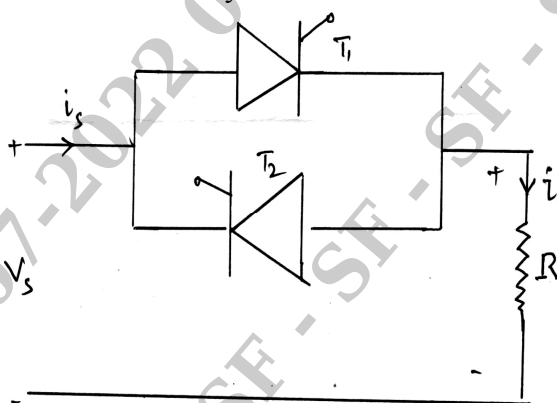


Fig Q5(c)

(06 Marks)

- 6 a. With the help of circuit diagram, explain the operation of single phase AC regulator using ON-OFF control. Derive the expression for rms value of load voltage. (08 Marks)
 b. Explain the operation of single phase bi-directional AC voltage controller for inductive load with the help of circuit diagram and waveforms. (08 Marks)
 c. Distinguish between ON-OFF control and phase control of AC voltage controller. (04 Marks)
- 7 a. With neat circuit diagram, explain the principle of operation of step up chopper. (06 Marks)
 b. Give the classification of choppers. Explain class E-chopper with circuit and quadrant diagram. (08 Marks)
 c. In the chopper circuit shown in Fig Q7(c), the average output voltage is 109V. The voltage drop across chopper switch when it is ON is $V_s = 2V$. The load resistor $R = 10\Omega$, $f = 1.5KHz$ and duty cycle ratio $\delta = 50\%$. Calculate the i) DC input voltage to the chopper ii) RMS output voltage.

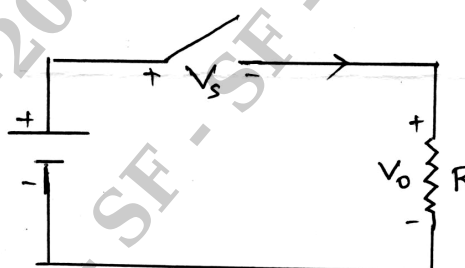

$R = 10\Omega$
 $f = 1.5KHz$
 $V_s = 2V$
 $\delta = 50\%$

Fig Q7(c)

(06 Marks)

- 8 a. With necessary sketches, explain the single phase transistorized current source inverter. (10 Marks)
 b. Explain the performance parameters of inverters. (06 Marks)
 c. Compare voltage source inverters and current source inverters. (04 Marks)
