

USN

--	--	--	--	--	--	--	--



10EC73

Seventh Semester B.E. Degree Examination, Dec.2019/Jan.2020

Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain the classification of power semiconductor switching devices, on the basis of control characteristics. (08 Marks)
 b. Explain different types of power converter systems with circuit and waveforms. (08 Marks)
 c. Draw symbol and characteristics of the following devices: i) SITH ii) SIT (04 Marks)

- 2 a. Using transient model of BJT, explain switching characteristics of power transistor. (10 Marks)
 b. The collective clamping circuit in Fig.Q2(b) has $V_{CC} = 100$ V, $R_C = 1.5 \Omega$, $V_{d_1} = 2.1$ V, $V_{d_2} = 0.9$ V, $V_{BE} = 0.7$ V, $V_B = 15$ V and $R_B = 2.5 \Omega$, $\beta = 16$. Calculate:
 i) Collector emitter clamping voltage V_{CE}
 ii) Collector event without clamping

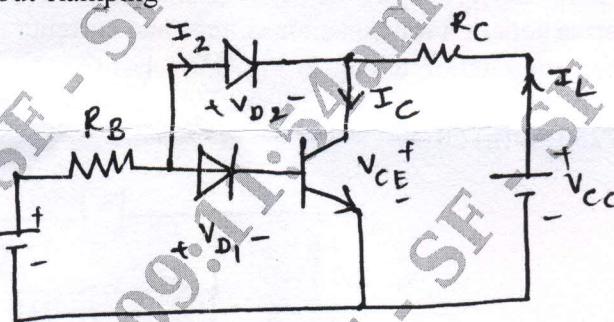


Fig.Q2(b)

(06 Marks)
(04 Marks)

- c. Compare the features of BJT and MOSFET. (04 Marks)
- 3 a. Using two transistor analogy, derive an expression for anode event of a SCR. (08 Marks)
 b. Briefly explain dynamic turn-ON and turn-off characteristics of SCR. (08 Marks)
 c. If the latching event of SCR shown in Fig.Q3(c) is 4 mA, find the minimum width of gate pulse required to turn-ON SCR. (04 Marks)

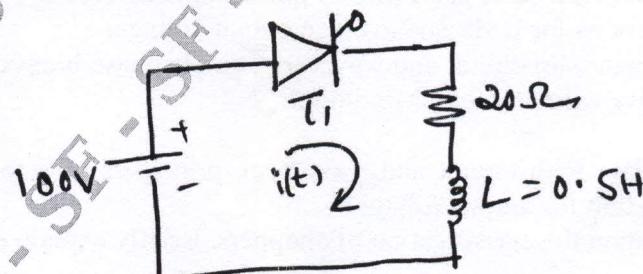


Fig.Q3(c)

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. The converter circuit shown in Fig.Q4(a) has resistive load of R and delay angle is $\alpha = \frac{\pi}{2}$, determine:
- Rectifier efficiency
 - Form factor FF
 - Ripple factor RF
 - Transformer utilization factor TUF
 - PIV of thyristor.

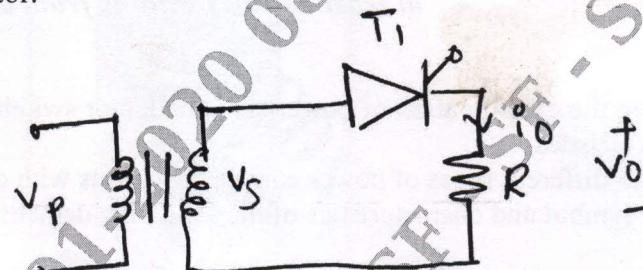


Fig.Q4(a)

(10 Marks)

- b. Explain with neat circuit and waveform, single phase full converter with R-load. Derive equation for V_{DC} and V_{rms} . (10 Marks)

PART - B

- 5 a. Explain the principles of self commutation circuit with necessary circuit and waveform. Derive equation for capacitor voltage and current. (10 Marks)
- b. The commutation circuit in Fig.Q5(b) has $C = 30 \mu F$ and inductance $L = 4 \mu H$. The initial capacitor voltage is $V_D = 200 V$. Determine the circuit turn-off time t_{off} if load current I_m is
- 250 A
 - 50 A.

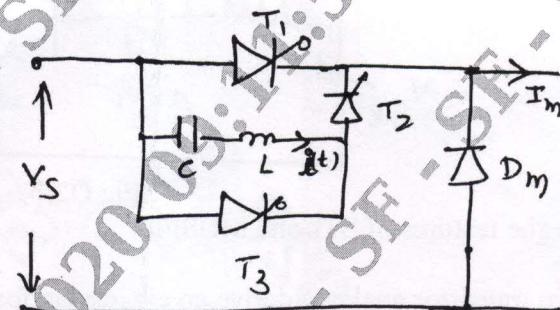


Fig.Q5(b)

(10 Marks)

- 6 a. Explain the basic principles of phase angle controller with neat circuit and waveform. Derive equations for RMS and average output voltage. (10 Marks)
- b. Explain with circuit and waveform, single phase bidirectional controller with resistive loads. Derive equation for RMS output. (10 Marks)
- 7 a. Explain with circuit and waveform, principles of step down chopper with R-load. Derive equation for output voltage. (10 Marks)
- b. Mention the classification of choppers. Briefly explain each type. (10 Marks)
- 8 a. Explain with circuit and waveform, single phase bridge inverter. (10 Marks)
- b. Explain with circuit and waveform, single phase current source inverter. (10 Marks)

* * * * *