



**Seventh Semester B.E. Degree Examination June/July 2019**

**Power Electronics**


Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting at least TWO questions from each part.**

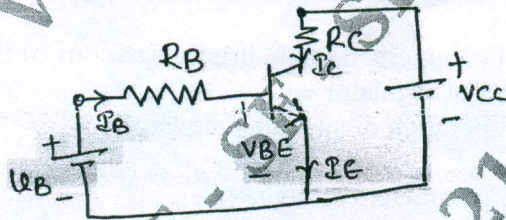**PART - A**

- 1 a. Explain five types of power electronic converter circuits briefly. Also indicate two applications of each type. (10 Marks)
- b. Give symbol, and characteristic features of the following devices: (10 Marks)
  - i) RCT      ii) GTO      iii) Triac      iv) SCR      v) IGBT
- 2 a. Give the comparison between BJT, MOSFET and IGBT. (06 Marks)
- b. What is the necessity of base drive control in a power transistor? Explain antisaturation control. (08 Marks)
- c. For a transistor switch shown in Fig.Q2(c):
  - i) Calculate the forced beta,  $\beta_F$  of transistor.
  - ii) If the manufacturers specified  $\beta$  in the range of 8 to 40, calculate the minimum overdrive factor (ODF)
  - iii) Obtain power loss  $P_T$  in the transistor.



$$\begin{aligned}
 V_B &= 10V, R_B = 0.75\Omega \\
 V_{BE(sat)} &= 1.5V \\
 R_C &= 11\Omega, V_{CC} = 200V \\
 V_{CE(sat)} &= 1V
 \end{aligned}$$

Fig.Q2(c)

(06 Marks)

- 3 a. Draw the two transistor model of a thyristor and derive an expression for the anode current in terms of the common base current gain  $\alpha_1$  and  $\alpha_2$  of the transistors. (09 Marks)
- b. What is the need for protection of thyristor? Explain how thyristors are protected against high  $\frac{di}{dt}$ . (06 Marks)
- c. Explain different methods to turn on a thyristor. (05 Marks)
- 4 a. What will be the average power in the load for the circuit shown in Fig.Q4(a), when  $\alpha = \frac{\pi}{4}$ . Assume SCR to be ideal. Supply voltage is  $330 \sin 314t$ . Also calculate the RMS power and the rectification efficient.

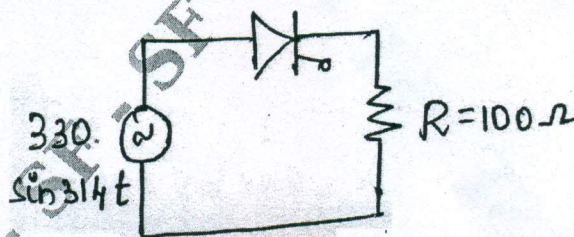


Fig.Q4(a)

(06 Marks)

- b. With a neat circuit diagram and waveforms, explain the working of a single phase full controlled bridge converter feeding highly inductive load. Derive the expression for the average output voltage and rms output voltage. (10 Marks)
- c. Compare full controlled and semi-controlled rectifiers. (04 Marks)

**PART - B**

- 5 a. With a neat circuit diagram and waveforms, explain complementary commutation. (10 Marks)
- b. In the resonant pulse commutation circuit, the supply voltage is  $V_s = 200$  V, load current  $I_o = 150$  A, the commutation inductance  $L = 4\mu\text{H}$  and commutation capacitance  $C = 20\mu\text{F}$ . Determine the peak resonant reversing current of thyristor  $T_3$  and turn OFF time  $t_{\text{OFF}}$  for  $T_1$ . Assume  $V_o = V_s$ . (10 Marks)
- 6 a. With relevant circuit and waveform, explain the principle of single phase fullwave AC voltage controller with resistive load. Derive expression for RMS output voltage. (10 Marks)
- b. A single phase FW ac voltage controller working on ON-OFF control has supply voltage of 230 V RMS, 50 Hz and load is  $50\ \Omega$ . The controller is ON for 30 cycles and OFF for 40 cycles. Calculate:
- ON or OFF time interval
  - RMS output voltage
  - Input power factor
  - Average and RMS thyristor current.
- (06 Marks)
- c. Compare ON-OFF controller and phase controller. (04 Marks)
- 7 a. Give the classification of choppers. Explain briefly each one of them. (10 Marks)
- b. Explain the working of boost regulator with waveforms. (06 Marks)
- c. Explain the principle of operation of step up chopper. (04 Marks)
- 8 a. Explain the performance parameters of inverters. (06 Marks)
- b. Explain the operations of single phase half bridge inverter. (08 Marks)
- c. Explain the working of variable DC link inverter. (06 Marks)

\*\*\*\*\*