

USN

--	--	--	--	--	--	--	--	--	--



10CS33

Third Semester B.E. Degree Examination, June/July 2015
Logic Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1 a. Define: i) Rise time ii) Fall time iii) Period and iv) Frequency. (08 Marks)
 b. What is an universal gate? List the universal gates and prove their universalities. (06 Marks)
 c. Write the verilog code for the circuit given below. (06 Marks)

 


Fig.Q.1(c)

- 2 a. Using K-map find the reduced SOP form of $f(A, B, C, D) = \sum M(5, 6, 7, 12, 13) + \sum d(4, 9, 14, 15)$. (05 Marks)
 b. What is a hazard? List the types of hazards and explain static-0 and static-1 hazards. (05 Marks)
 c. Simplify the following using Mc-Cluskey method $F = \sum M(0, 1, 2, 8, 10, 11, 14, 15)$. (10 Marks)
- 3 a. Implement the following function using a 8:1 multiplexer: $f(a, b, c, d) = \sum M(0, 1, 5, 6, 8, 10, 12, 15)$. (08 Marks)
 b. Realize the following function using the 3:8 decoder $F_1(A, B, C) = \sum M(1, 2, 3, 4)$, $F_2(A, B, C) = \sum M(3, 5, 7)$. (06 Marks)
 c. What is a magnitude comparator? Explain with a neat block diagram an n-bit magnitude comparator. (06 Marks)
- 4 a. With a neat block diagram, explain the working of a Master-Slave JK flip flop. Also write its truth table. (10 Marks)
 b. Define: i) Flip flop ii) Hold time iii) Set up time iv) Characteristic equation. (04 Marks)
 c. Calculate the clock cycle time for a system that uses a clock, that has a frequency of
 i) 10 MHz ii) 50 MHz iii) 750 kHz. (06 Marks)

PART – B

- 5 a. Draw the logic diagram of a 4-bit serial in serial out shift register using J-K flip flop and explain. (08 Marks)
 b. Explain briefly serial adder with a neat sketch. (08 Marks)
 c. Write a verilog code for switched tail counter. (04 Marks)



- 6 a. Briefly explain 3-bit binary ripple up-counter. Also write the truth table and waveform. (10 Marks)
- b. Design a Modulo-5 up counter (synchronous) using J-k flip flop. (10 Marks)

- 7 a. With neat block diagrams compare Mealy model and Moore model of sequential logic system. (08 Marks)
- b. Draw the ASM chart for vending machine problem using Mealy model. (12 Marks)

- 8 a. Explain the concept of "Successive approximation" of a A/D converter. (10 Marks)
- b. Draw a binary ladder network for a digital input 1000 and obtain its equivalent circuit. (10 Marks)

* * * * *

Highly confidential document EDC - 184, @ 23-06-2013