



USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2019
Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. With a neat diagram, explain the working of TTL NAND gate. (06 Marks)
- b. What are the advantages of HDL? Explain the types of models in HDL with an example of each. (08 Marks)
- c. Consider the following logic circuit of Fig.Q1(c). Write the verilog structural code for the same. (06 Marks)

 


Fig.Q1(c)

- 2 a. Using K-map, simplify the Boolean expression $F(A, B, C, D) = \sum m(0, 3, 4, 5, 6, 7, 11, 15) + dc(2, 8, 9, 10, 12, 13)$ Implement the simplified equation using NAND gates. (06 Marks)
- b. For the following K-map of Fig.Q2(b) give SOP and POS form that do not show static 0 or static 1 hazard. (06 Marks)

	\bar{C}	C
$\bar{A} \bar{B}$	1	1
$\bar{A} B$	0	0
$A \bar{B}$	1	0
$A B$	1	0

Fig.Q2(b)

- c. Reduce the following function using Quine McClusky method. $F(A, B, C, D) = \sum m(1, 4, 6, 8, 9, 10, 11, 12, 13) + dc(3, 15)$ Implement the simplified equation using NOR Gates. (08 Marks)
- 3 a. Define multiplexer and draw the logic diagram of 4:1 MUX. Implement the Boolean function $F(A, B, C, D) = \sum m(1, 7, 9, 10, 12, 13, 14, 15)$ using 8 to 1 MUX. (06 Marks)
- b. Draw a ROM circuit that realize the Boolean functions.

$$Y_3 = \bar{A} B \bar{C}$$

$$Y_2 = A \bar{B} C + ABC$$

$$Y_1 = A \bar{B} C + \bar{A} B C + ABC$$

$$Y_0 = \bar{A} B \bar{C} + \bar{A} B C + A B \bar{C} + ABC$$

(07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Define an encoder. Design a priority encoder the truth table of which is shown in Fig.Q3(c) (07 Marks)

Input				Output	
S	X ₁	X ₂	X ₃	A	B
0	X	X	X	0	0
1	1	X	X	0	1
1	0	1	X	1	0
1	0	0	1	1	1
1	0	0	0	0	0

Fig.Q3(c)

- 4 a. What is meant by edge triggered flip flop and explain the terms propagation delay, setup time and hold time of a flip flop. (04 Marks)
- b. What is excitation table? Write the characteristics equation, state transition diagram and flip-flop excitation table for JK flip-flop. Also write the verilog code for SR latch. (07 Marks)
- c. Convert D flip-flop to SR flip flop and draw the logic diagram. (04 Marks)
- d. Analyse the following circuit of Fig.Q4(d) and indicate what it does. (05 Marks)

 


Fig.Q4(d)

PART - B

- 5 a. With a neat diagram, explain 4 bit parallel in serial out shift register using D flip flop. (08 Marks)
- b. What is the difference between serial in serial out and parallel in parallel out shift register? (02 Marks)
- c. Explain with neat diagram and waveform 4 bit shift register can be used as ring counter and Johnson's counter. (08 Marks)
- d. How long will it take to shift an 8 bit number into a 54164 shift register if the clock is set at 10 MHz. (02 Marks)
- 6 a. What is modulus of a counter? Design synchronous decade counter using JK flip-flop. (08 Marks)
- b. What are decoding gates? What is the primary cause of glitches that occur at the output of a decoding gate used with a ripple counter? What is one method to eliminate these glitches? (03 Marks)
- c. Define duty cycle. What is the value of duty cycle for an asymmetrical signal if the waveform is high for 2 ms and low for 5 ms? (03 Marks)
- d. With a neat diagram and waveform, explain 3 bit asynchronous updown counter. (06 Marks)



- 7 a. Design a sequence detector using Mealy model that detects three consecutive zero's from an input data stream, x and signals detection by making output, y = 1. (06 Marks)
- b. Differentiate between Mealy machine and Moore machine. (02 Marks)
- c. Reduce state transition diagram of Fig.Q7(c) by (i) Row elimination method and (ii) Implication table method. (12 Marks)

 


Fig.Q7(c)

- 8 a. Draw a 4 bit D/A converter using R/2R resistors and explain the working. (06 Marks)
- b. What is accuracy and resolution of D/A converter? What is the resolution of a 12 bit D/A converter which uses a binary ladder? If the full scale output is +10V, what is the resolution in volts. (04 Marks)
- c. Explain Dual slope A/D conversion. (10 Marks)
