

USN

--	--	--	--	--	--	--	--	--	--



10CS33

**Third Semester B.E. Degree Examination, Dec.2019/Jan.2020**  
**Logic Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART - A**

- 1 a. What is the difference between  
(i) Analog and digital signals (ii) Ideal and Practical waveform (04 Marks)
- b. Implement the following function using only universal gates  
 $(\bar{A} \cdot \bar{B}) + \bar{C}$  D (06 Marks)
- c. Consider the black box test circuit has following logic circuit shown in Fig.Q1(c). Write verilog structural code for the given circuit. (06 Marks)

 


Fig.Q1(c)

- d. Prove that De Morgan's two theorems with the help of truth table. (04 Marks)
- 2 a. Design logic circuit for the sum of product equation  
 $Y = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$   
Write a general structure of Karnaugh map for four input F(A, B, C, D) (05 Marks)
- b. With example explain entered variable. Write a truth table for entered variable map shown in Fig.Q2(b). (05 Marks)

	$\bar{B}$	B
$\bar{A}$	0	$\bar{C}$
A	C	1

Fig.Q2(b)

- c. Simplify the following logic equation using Karnaugh map draw circuit using only NAND gates.  
 $F(A, B, C, D) = \sum m(7) + dc(10, 11, 12, 13, 14, 15)$  (05 Marks)
- d. What is Hazard? With graph explain any one Hazard. (05 Marks)
- 3 a. What is multiplexer and demultiplexer? With figure explain 2 input multiplexer and 2 output demultiplexer. (04 Marks)
- b. With figure explain 4 input exclusive – OR gate and also write truth table for four input exclusive OR gate. (04 Marks)
- c. Explain encoder. Design an encoder which converts decimal number to BCD number. (06 Marks)
- d. Design 7-segment decoder using programmable logic array. (06 Marks)



- 4 a. With timing diagram, describe logic circuit which generate series of negative and positive narrow pulses. (05 Marks)
- b. With figure, explain four bit data storage by using D flip-flop. (05 Marks)
- c. With transition diagram, explain finite state machine of all the flip-flop by using two states. (06 Marks)
- d. Design S-R flip-flop by using D-flip-flop. (04 Marks)

**PART - B**

- 5 a. With neat diagram, explain serial in and serial out by using J-K flip-flop. Show how number 0100 is entered serially in a shift register using state table. (10 Marks)
- b. Design Johnson counter by using D flip-flop. Write verilog code for a Johnson counter. (10 Marks)
- 6 a. Explain in detail mode 5 binary counter by using JK flip-flop. (10 Marks)
- b. Explain digital clock with a block diagram. (10 Marks)
- 7 a. Reduce Moore model of Fig.Q7(a) by using
  - (i) Row elimination method
  - (ii) Implication table method, with partition table. (10 Marks)

 


Fig.Q7(a)

- b. Draw algorithm state machine for vending machine problem by Mealy model. (10 Marks)
- 8 a. With neat sketch, explain sample and hold circuit of D/A conversion. (10 Marks)
- b. With neat diagram, explain analog to digital conversion by using simultaneous conversion method. (10 Marks)

\*\*\*\*\*